Latches and Flip-Flops

Hanwool Jeong hwjeong@kw.ac.kr

Contents

- Brief introduction to memory
- Conventional latches and flip-flop circuits & issues
- Improved flip-flop circuits

Memory Operation

- Processor calculates
- Memory can hold/read/write data



Form of Binary Data

- Memory element stores data in binary form : "0" and "1"
- Memory should be able to be in two electrically separable states.





Memory element should hold/write/read two possible states

Let's Make A Memory Element : Hold Two Possible States

- Remember: Memory should **hold**/write/read **two states**
- How can we implement two electrically distinguishable states in the digital circuit?



→ Can we use a capacitor as a memory? How about writing data?

Problem of Capacitor Memory

Can you change the following state into data "0"? → NO



Addition of "Switch" for Read/Write



Let's Make A Memory Element : Write Two Possible States

• Let's write data "0" to memory bitcell initially storing "1"



1T1C DRAM Bitcell

• Dynamic Random Access Memory (DRAM) Bitcell





Limitation of DRAM

- Suppose that data "1" is stored in the DRAM bitcell
- What if there is a leakage current or Noise?
 Data can be "dynamically" changed



Can We Solve the Problem?

- How about using digital logic?
- It can yield "0" or "1" logic by 0V and 3V, respectively.
- But the input should be provided to realize it.
- → How can we handle this?

Revisit Regeneration Feature of Inverter

 While the input can have arbitrary values, output can become 3V or 0V



Cross-coupled Inverter as A Memory



Robustness of Cross-Coupled Inverters

 Cross-coupled inverter is free from the problem which DRAM suffers from



Cross-coupled Inverters as Memory?

Can you change the following state into data "0"? → NO



Data "1"

Revisit: What We Did for DRAM Bitcell



Enabling Read/Write Operation to Cross-Coupled Inverters



Cross-Coupled Inverter Cross-Coupled Inverter + Two nMOSFET w/ 2+1 externally controllable lines

Write Operation



Write Operation Waveform



6T SRAM Bitcell

- Static Random Access Memory (SRAM) Bitcell
- "Static" means invariant memory storage operation over time



	Memory Controller							
Constant of								
Misc HO	Core	Core	Q, a a a	Core	Core	PCIe		
		Share	d L3	Cache				

Need for Sequential Circuit & State; Smartphone Auto Brightness Control

• We need clock (synchronous) and states (sequential).





Sequential Circuit

- State is stored in memory, which is to be used at later time.
- Inputs/States/Outputs are all formed in binary.



Synchronous Sequential Circuit

- Storage elements in clocked sequential circuits are called flip-flops, which is a binary storage device storing one bit.
- Flip-flop updates the state every rising edge of clock. Then, the state is feedback to the combinational logic.



How Can We Store States?

- States should be used mapped into binary numbers.
- If we have 50 possible states, then we should allocate 6 bits to represent a state. That is, we need six flip flops.
- Then, how does flip-flop or memory elements for storing state look like?
- It should be able to perform three main operations
 - The state should be able to be **stored (hold)**.
 - The state should be able to be **changed** to what is intended (write)
 - The state should be able to be detected (read).

Revisit SRAM Write Operation

• It requires the differential data lines and suffers from contention



Initial Thought & Latch

- Compared to SRAM which necessitates high density, a flip flop can be implemented with larger area.
- First, let's focus on implementing a memory element that is
 - 1) Free from the contention during data update.
 - 2) Writable only when clock is high.
- We will define three nodes for this memory element, and call it as a latch

Q is updated to D for Clk = 1
 Q holds the old value for Clk = 0

Let's Make A Latch

- How can we realize the following?
 - 1) Q is **updated** to D for Clk = 1
 - 2) Q holds the old value for Clk = 0



TG based D-Latch

- You can utilize tri-state inverter
- You can separately additionally output inverter to improve drivability.







You Can Start From NAND2 or NOR2

NAND2 and NOR2 become inverter when



• NAND or NOR yield fixed output independently to other inputs when



Cross-Coupled Inverters With NAND2 or NOR2

- For data hold, the cross-coupled inverters should be implemented.
- How can you configure the cross-coupled inverters using NAND2 or NOR2?



Holding & Updating Data



Updating Data Only When Clk = 1

- Focus on the target operation
 - Clk = 1 : Update (or we say this state as "transparent")
 - Clk = 0 : Hold (or we say this state as "opaque")



Preventing Forbidden State



Clk	D	
0	0	Hold
0	1	Hold
1	0	Q=0
1	1	Q=1

Which Do You Prefer?







Operational Waveforms of Latch



Latch to Flip-Flop

- Note that our target operation is to update D at the rising edge of clock, not Clk = 1.
- How can we implement this?



Ideation

- The latch reflects D into Q only when Clk = 1
- The aim of flip-flop is to reflect D into Q only at the rising edge of Clk.
- Then, how about shortly enable the latch at the rising edge of clock?
- That means,



Pulsed Latch or Pulse-Triggered Flip Flop

Pulsed latch or Pulse-triggered flip-flop



Conventional TG Pulsed Latch (TGPL)



What if?

• Ideally, what should Q be?



Large Pulse Width Constraint for Variation Aware Design



S. D. Naffziger, et al., "The implementation of the Itanium 2 microprocessor," in *IEEE Journal of Solid-State Circuits*, vol. 37, no. 11, pp. 1448-1460, Nov. 2002.





Hold Time Issue in Pulsed Latch (Race Condition)

• How can we handle this? We need hold time constraint for D!



• Hold time is the minimum amount of time the data input must be unchanged after the clock edge for stable sampling

Ideation

Key: D = Q(t) while D \leftarrow Q(t+1) only at the rising edge

 Okay, let's accept Q(t+1) and store it before clock becomes high inside the flip-flop.

→Q(t+1) must be disconnected to Q (∵Q should be kept with Q(t)).
 →Q(t+1) must be connected to D to accept and store it

- At the rising edge of clock, stop accepting D and transfer Q(t+1) to the output Q.
 - \rightarrow Q(t+1) must be connected to Q.
 - \rightarrow Q(t+1) must be disconnected to D.
- Then, until the next rising edge of clock,

→Q(t+1) must be disconnected to Q and Q(t+1) must be connected to D to accept and store it.

→Q(t) must be kept and stored

Circuit Design for Flip Flop

- When Clk = 1, that is, just before clock rises
 - Q(t+1) is dynamically changed according to D (D acceptation) while it is disconnected Q.
 - Q(t) is stably & unchanged stored and connected to Q.

Clock

Thus, we need two latches





TR Level Schematic of Conventional TG Flip Flop (TGFF)

 We also call this type of structures as master-slave latch based Flip-Flop



Operation of TGFF





What if?

• Ideally, what should Q be?



Failing to Capture D @ Clk Rising

- During Clk=0, the master latch should capture low D.
- If Clk rises too quickly after D falls, D may not be able to reflected to the master latch.



→ How can we handle this?

Setup Time Issue in TGFF

• We need a setup time constraint for flip-flop.



• Setup time is the minimum amount of time the data input must be stable before the clock edge for stable latching.

Summary of Issues in Conventional FF (TGPL and TGFF)

- In TGPL, the generated pulse should have sufficiently large width to guarantee the appropriate development of internal nodes of the latch.
- Enlarged pulse width may reflect D change after Clk edge inside the latch, which incurs the malfunction.
- Thus, D should be kept unchanged after the Clk rising edge, meaning the TGPL have a finite positive hold time constraint.
- In TGFF, the master latch a finite time to capture D before Clk edge because it takes times for the internal node to change.
- Thus, if D changes right before Clk edge may not be reflected to the master latch, meaning TGFF requires a finite positive setup time constraint.

Any Way We Can Mitigate Conventional FF Issues?

- There may be two approaches
 - 1) Reducing hold time for TGPL.
 - 2) Reducing setup time TGFF.
- Let's see how 1) can be implemented thru a circuit design.

Ideation

- The cause of large hold time in TGPL is pulse width may unnecessarily large in many TGPLs, although it is inevitable to cover the slow TGPL.
- We can reduce the hold time if we can generate the pulse width as the exact time it is required for a TGPL.
- What is the meaning of the exact time?
- \rightarrow That is the time required for Q to be captured properly.
- \rightarrow As soon as Q is well developed, we disconnect D from the latch.
- Is there any way we can disconnect D from the internal nodes of the latch, right after the capture is performed properly?

Fitted Delay Generation is Key!





S. Luo, et al, "An Adaptive Pulse-Triggered Flip-Flop for a High-Speed and Voltage-Scalable Standard Cell Library," in *IEEE Transactions on Circuits and Systems II: Express Briefs*, vol. 60, no. 10, pp. 677-681, Oct. 2013.

Local variation can still exist!

Let's Sense Whether the Q is Captured

- How can we sense whether Q is properly developed?
- We can sense whether Q becomes same with D.



TRANS Generation Through XNOR

- We saw various XNOR and XOR. Static XNOR/XOR is bulky.
- What we have to do is compare D & Q after the rising edge.
- → Thus, we can utilize dynamic XNOR



Hold Time Issue Arises When..

- How about disabling effect of falling D at the rising edge of Clk?
- → Dynamic circuit has the monotonicity!



Ideation (cont'd)

- Once X falls, D=1 should be captured.
- How about if D=0? We can use a dual dynamic circuit!
- Once Y rises, D=0 should be captured.
- As soon as D is sensed, the input D should be blocked/disconnected from the latch. How?
- → Y rise blocks D to X path, X fall blocks D to Y path (Why?)



Ideation

• Y rise blocks D to X path, X fall blocks D to Y path



Circuit Completion; Q Driving

- X = 0 means D = 1 at the Clk edge, thus Q should be 1.
- Y = 1 means D = 0 at the Clk edge, thus Q should be 0.



Circuit Completion; Latching

- Q should be latched for low Clk.
- X or Y should be latched for high Clk.



Complete Design for Self Shut-off Pulsed Latch





Summary

- TGPL has the limitation of large hold time constraint due to inevitable large pulse width.
- To reduce the hold time in TGPL, the adaptive pulse triggering techniques have been proposed.