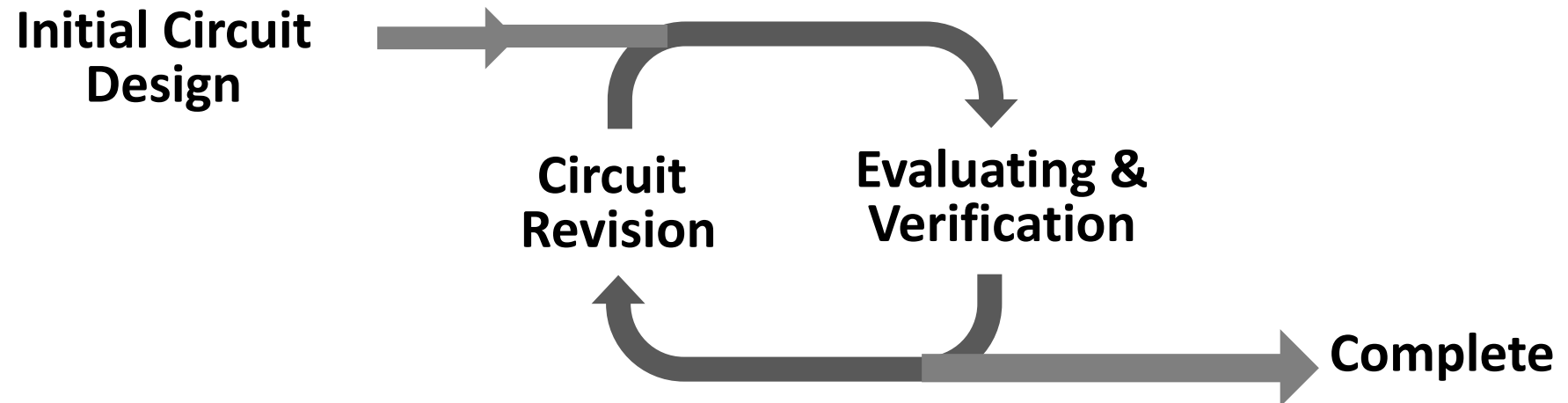


How Do You Think IC Design Flow is Like?

- There must be a target circuit spec that should be satisfied.
- How can we design a circuit that meet such spec?




- How can you evaluate and verify circuit design?

Make An IC Chip!


- How long does it take to get an IC chip?
➔ Typically 6-8 weeks at least
- How much does it cost?

How Can We Predict Circuit Performance?

- Circuit simulation do work but

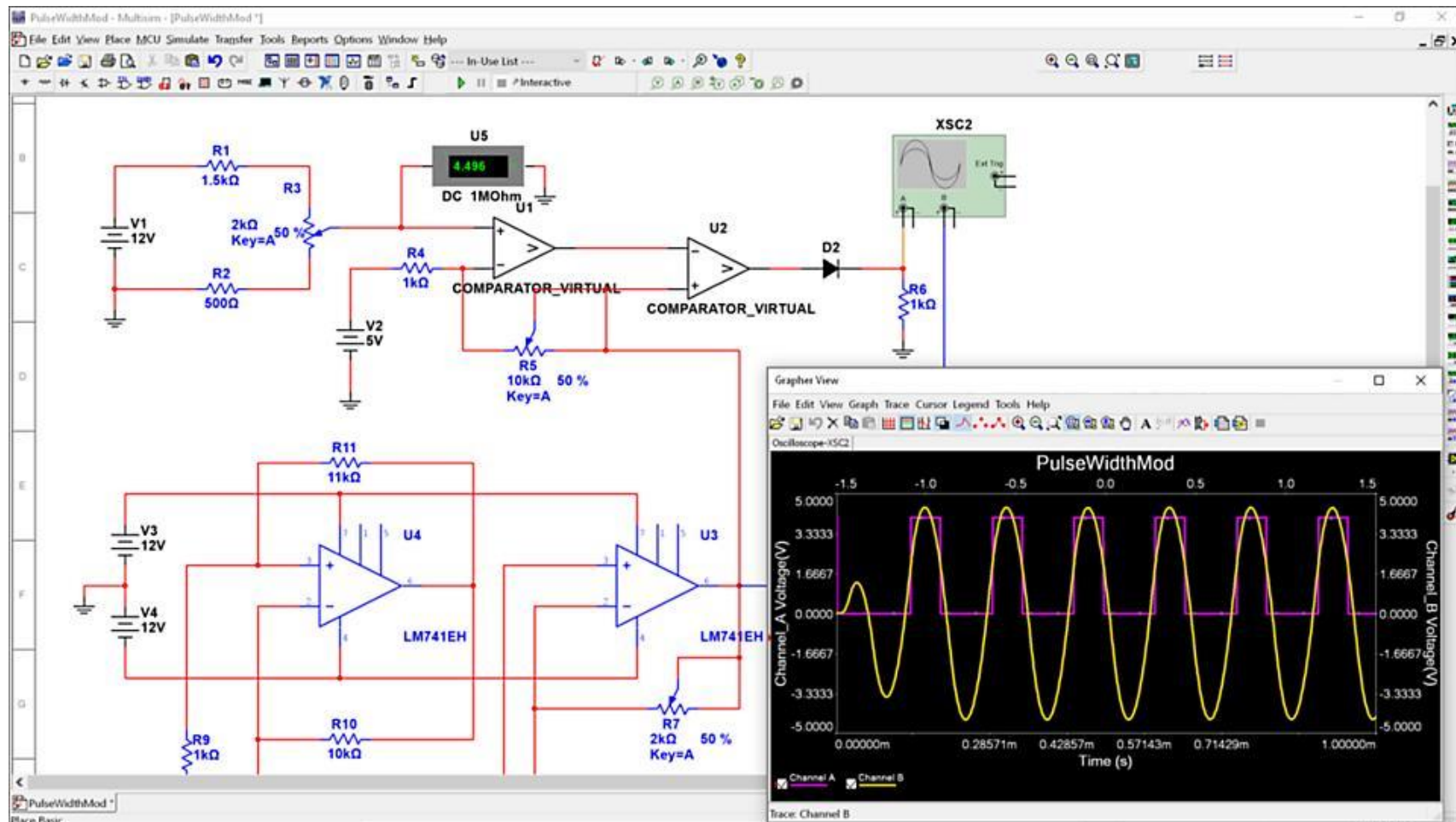

Typical IC Design Flow

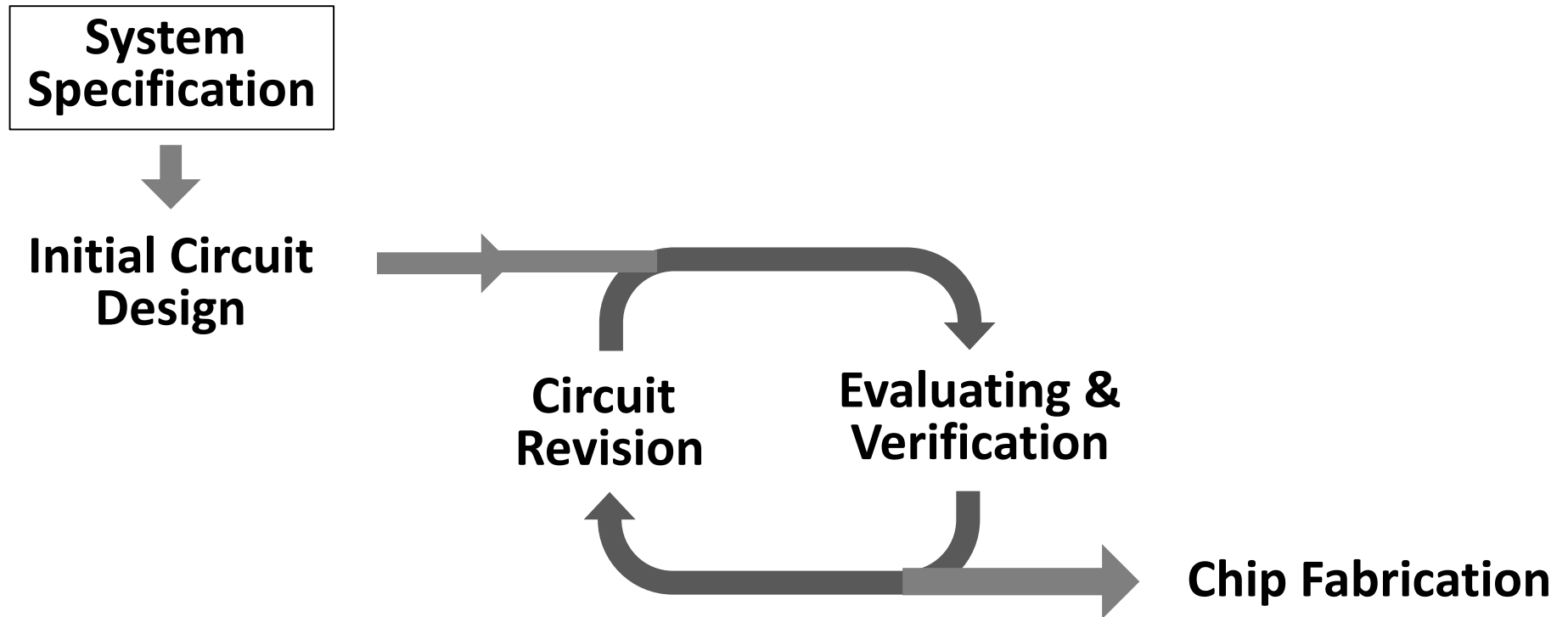

Role of Circuit Designer

- A circuit designer should be able to estimate the circuit performance analytically without simulation.
 - It does not mean you should estimate the circuit performance 100% accurate in quantitative respect. (Simulation or chip measure can do this)
 - Instead, you can say which is better design and why it is better to make a decision without simulation.
 - Then, you can solve the problem in circuit design area.
- ➔ Is there any tool that can give circuit designers a good insight on circuit speed?

Delay

Hanwool Jeong

hwjeong@kw.ac.kr

Contents

- Introduction
- RC delay model
- Linear delay model
- Logical efforts of paths

Introduction


- ✓ How can we quantify the circuit speed?

Revisit Source of Delay

- A circuit operation takes time because
 - Capacitance exists everywhere in a real circuit and
 - The capacitance cannot change its voltage instantaneously
- If a capacitance C is charged/discharged with a current I ,
$$I = C \, dV/dt$$
- How can we determine the delay in a circuit?

 Example; Transient Response in An Inverter Drives an Inverter

- When the rising input is applied to A, Y would fall





- To derive the A-Y delay, we can find V_Y vs. time
➔ **Transient response**
 - Derive the capacitance of Y node, C_Y
 - Then, $C_Y(dY/dt) = I_{MP} - I_{MN}$
 - According to V_A range and V_Y ranges ➔ Only numerical solution
 - The time when $V_Y = V_{DD}/2$ can be determined as the delay

What Really Matters ...

- Working out the full model is tedious and offers little insight.
- Leave it to simulation tools to derive an accurate transient response and delay.
- Instead, we need a much simpler model (high efficiency) with endurable accuracy.

Remember?

- They are both OR2. Which is faster?

  


RC Delay Model


- ✓ Approximating nonlinear MOSFET characteristics

RC Circuit?

 - We can derive the transient response of V_Y in the following 1st order RC circuit, where V_Y is initially 0V.




Delay in From 1st Order RC Circuit

 

Approximate 1; Effective Resistance

- Let's treat a MOSFET as a conditionally connected resistor.
 - And the value of resistance would be $R \propto L/W$.
 - In many cases, L is fixed with minimum length, thus $R \propto 1/W$.
- ➔ Defining unit-width MOSFET as R is useful. Then, when $W = kW_{\text{unit}}$ the effective resistance is R/k .

 Accurate value may not be important. Why?



Approximate 2; Gate and Diffusion Capacitance

- Let's assume that in unit-width MOSFET

$$C_{\text{gate}} = C_{\text{drain}} = C_{\text{source}} = C$$


- Then a MOSFET with k time of unit width has

$$C_{\text{gate}} = C_{\text{drain}} = C_{\text{source}} = kC$$

- What if L is increased?


Equivalent RC Circuits; Inverter

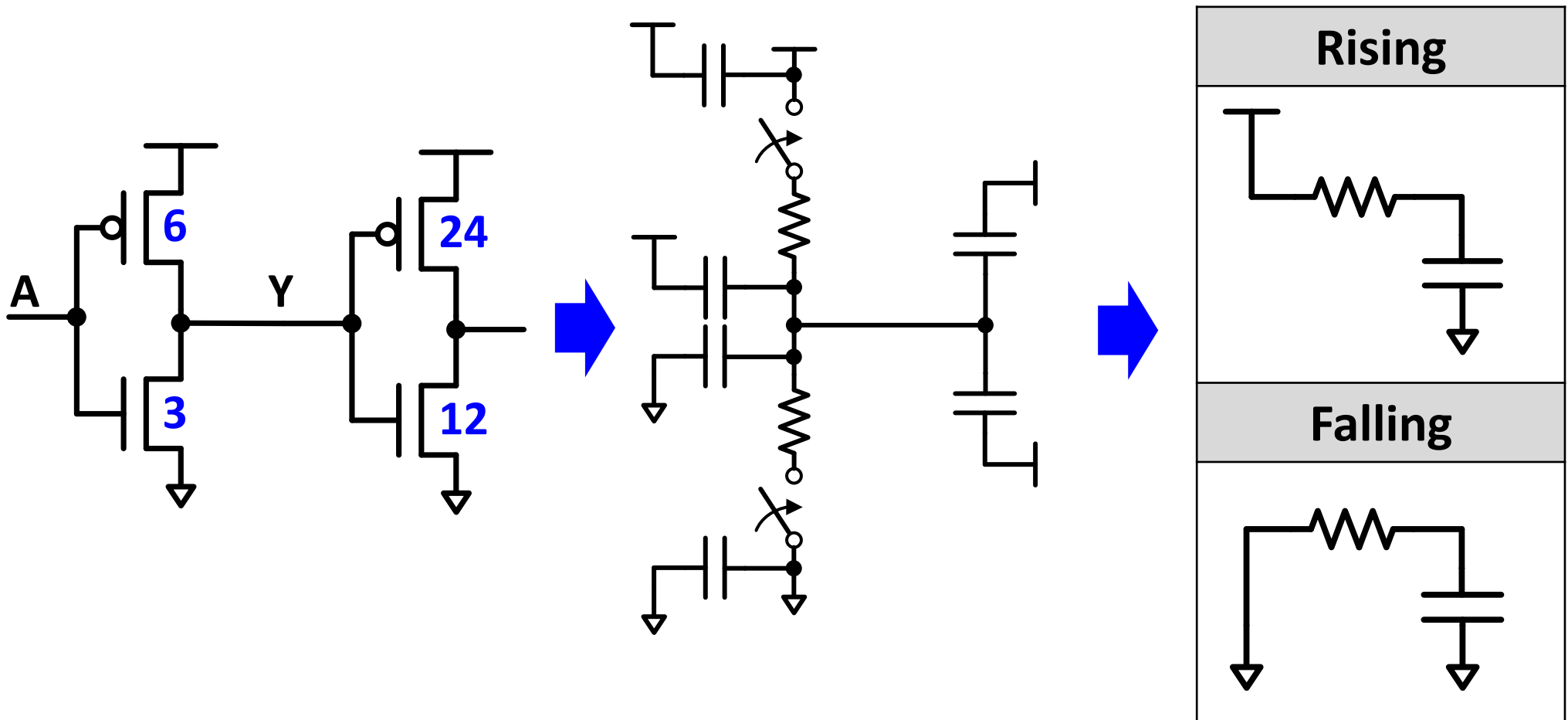- Suppose that we are interested in the time taken to change Y




Effect of Wire?

 - Wire can have capacitance and resistance as well.




Equivalent RC Circuits; NAND2

 - How should pMOSFET and nMOSFET size ratio be?
- What is the equivalent RC model for NAND2 fall delay?



 Transient Response of 2nd Order RC System



$$V_{\text{out}}(t) = V_{DD} \frac{\tau_1 e^{-t/\tau_1} - \tau_2 e^{-t/\tau_2}}{\tau_1 - \tau_2}$$



$$\tau_{1,2} = \frac{R_1 C_1 + (R_1 + R_2) C_2}{2} \left(1 \pm \sqrt{1 - \frac{4R^* C^*}{[1 + (1 + R^*) C^*]^2}} \right)$$

$$R^* = \frac{R_2}{R_1}; \quad C^* = \frac{C_2}{C_1}$$

First order Approximation

- When $R_1 = R_2$ and $C_1 = C_2$, $\tau_1 = 2.6RC$ and $\tau_2 = 0.4RC$ we can say $\tau_1 \gg \tau_2$ we can approximate it with first order with
  
$$\tau = \tau_1 \doteq \tau_1 + \tau_2 = R_1 C_1 + (R_1 + R_2) C_2$$



Elmore Delay

- Generalization of RC tree delay,

$$t_{pd} = \sum_i R_{is} C_i$$

t_{pd} = propagation delay


C_i = the capacitance of the node

R_{is} = resistance sum in the path of source from the node




Revisit 2nd order RC System

- Find Elmore delay of Y

$$t_{pd} = \sum_i R_{is} C_i$$


 


Can You Imagine RC Tree?

   


Estimating Delay of Inverter

  - Find Elmore delay of A to Y when a unit inverter shown in the left drives m identical unit inverters
- What if width is increased by k -times?
- What if R and C are given as $10\text{k}\Omega$ and $C = 0.1\text{fF}$, respectively?



Fan-out and Normalized Delay

 - Fanout (FO) means how many identical circuit a circuit drives



- When τ is defined as the FO1 inverter delay without parasitic cap, $\tau = 3RC$.
- Defining normalized delay is useful to express it with process-independent term so that circuits can be compared only based on their topologies.

$$d = t_{pd}/\tau$$


Can We Define Fanout When Different Logics Are Connected?

- We can generally define fan-out as

$$h = \frac{C_{out}}{C_{in}} = \text{fan out}$$

Normalized Delay

 - Can you express the following circuit with normalized delay?




Propagation & Contamination Delay

- Propagation delay time t_{pd}
= **maximum** time from the input crossing 50% to the output crossing 50%
- Contamination delay time t_{cd}
= **minimum** time from the input crossing 50% to the output crossing 50%


 
Example; NAND3

- Find t_{pdf} , t_{pdr} , t_{cdr} , t_{cdf} of the following NAND3 when
 - The effective resistance and gate cap of unit width MOSFET are R and C , respectively.
 - The following NAND3 drives m identical NAND3 gates.





Can You See The Difference?

  - They are both FO4 but differ in the normalized t_{pd} .



We Roughly See the Effects of...

 
 


➔ Can you generalize this respect and develop a model ?

Linear Delay Model

- ✓ Extension RC delay model for taking into account fanout and logic complexity

How Can We Consider Fan-out?

  

Delay for
Parasitic Cap
Independent to load

Delay for
Load Cap
Depends on **fanout**

Normalized Propagation Delay Model

- We can develop the following model in terms of normalized delay:


$$d = f + p$$

where

f = effort delay or stage effort

p = parasitic delay

 - How can we take into account the effect of $W_{\text{load}}/W_{\text{driver}}$ into f ?




Delay for	Delay for
Parasitic Cap	Load Cap
Independent to load	Depends on fanout

Let's Focus on Stage Effort

- When we define the normalized delay, $d=1$ means FO1 unit inverter delay without parasitic delay.
- Then how about FO2, FO3, FO4? If it is not unit inverter?
- Then can't we just define f as follows?

$$f = \frac{C_{out}}{C_{in}} = \text{fanout} = \text{electrical effort}$$

- No. what if

 

Now It is Time to Think How We Consider


- In the previous model of

$$d = f + p$$

in f and p , there should be not only $W_{\text{load}}/W_{\text{driver}}$ effect but also that of the logic complexity.



- We can just start from directly derive the delay ① vs. ②, and **feel** the difference

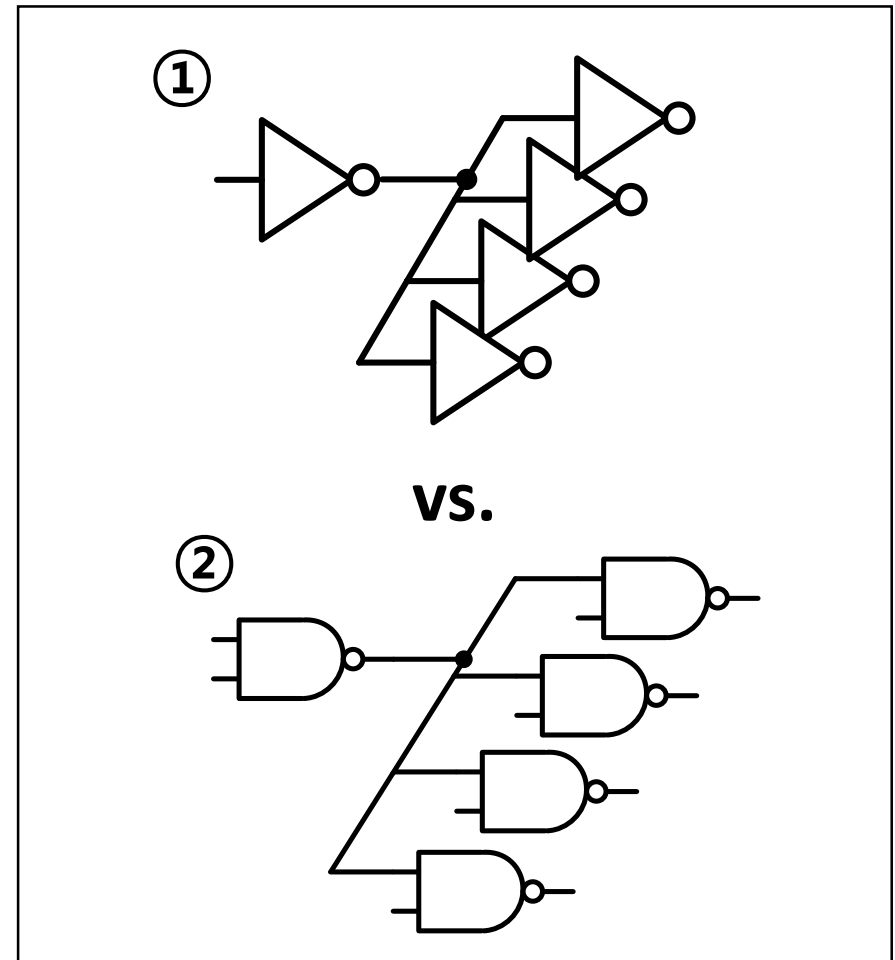➔ Then, we can may find how the model should look like.



Compare Delay

- And feel the difference

  

- Note that falling & rising strength are matched
- In $d = f + p$,

f is increased by times

p is increased by times

Refining Model

- In the previous model of

$$d = f + p$$

- If we define fan-out (=electrical effort) as h

$$h = C_{\text{out}}/C_{\text{in}}$$

- Then, we can make

$$d = g_{\text{logic}}h + p_{\text{logic}}$$



- Or simply,

$$d = gh + p$$

where g is **logical effort** and p is **parasitic delay**

Logical Effort g ?



- Where does it come from?

  

- It is attributed to the gate cap increase for matching the driving current.
- Definition: the ratio of the input capacitance of the gate to the input capacitance of an inverter that can deliver the same output current.
- Can you predict g of NAND3, NAND4, or NOR2, NOR3, NOR4, etc.?

Parasitic Delay for Various Logics?

- Where does it come from?

  

- It is attributed to the drain cap increase for matching the driving strength and the number of MOSFETs
- Definition: the delay of the gate when it drives zero load.
- Can you predict p of NAND3, NAND4, or NOR2, NOR3, NOR4, etc.?


g and p for Various Logics

Gate Type	Number of Inputs				
	1	2	3	4	n
inverter	1				
NAND		$4/3$	$5/3$	$6/3$	$(n + 2)/3$
NOR		$5/3$	$7/3$	$9/3$	$(2n + 1)/3$

Gate Type	Number of Inputs				
	1	2	3	4	n
inverter	1				
NAND		2	3	4	n
NOR		2	3	4	n

Normalized Delay vs. Fanout


- $d = gh + p$

 

Drive



- Generally, drive x is defined as

$$x = C_{in}/g$$

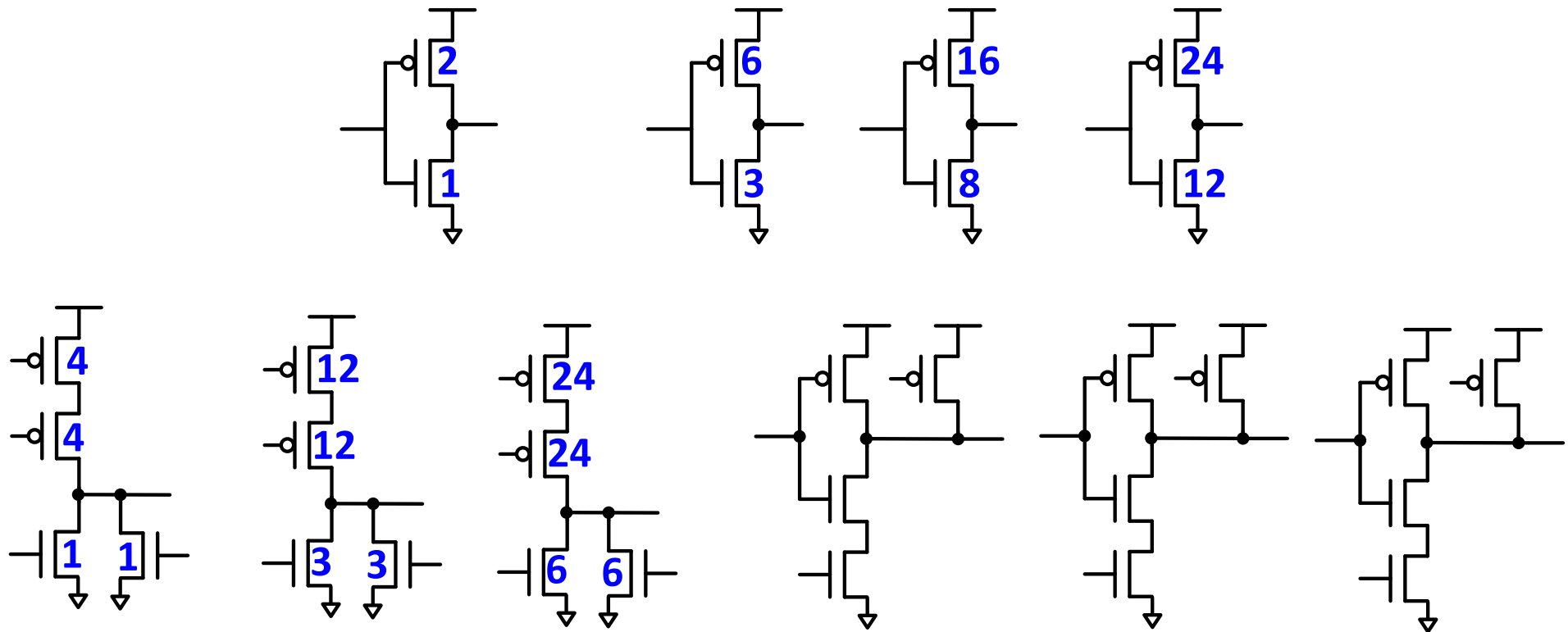

Methodology to Derive g , p and h Generally

  - Refer the unit inverter and start from deriving g by its definition of “the ratio of the input cap of the gate to the input cap of an inverter that can deliver the same output current.”




Logical Effort of Paths

- ✓ Path delay characterization and Optimization


Delay Optimization

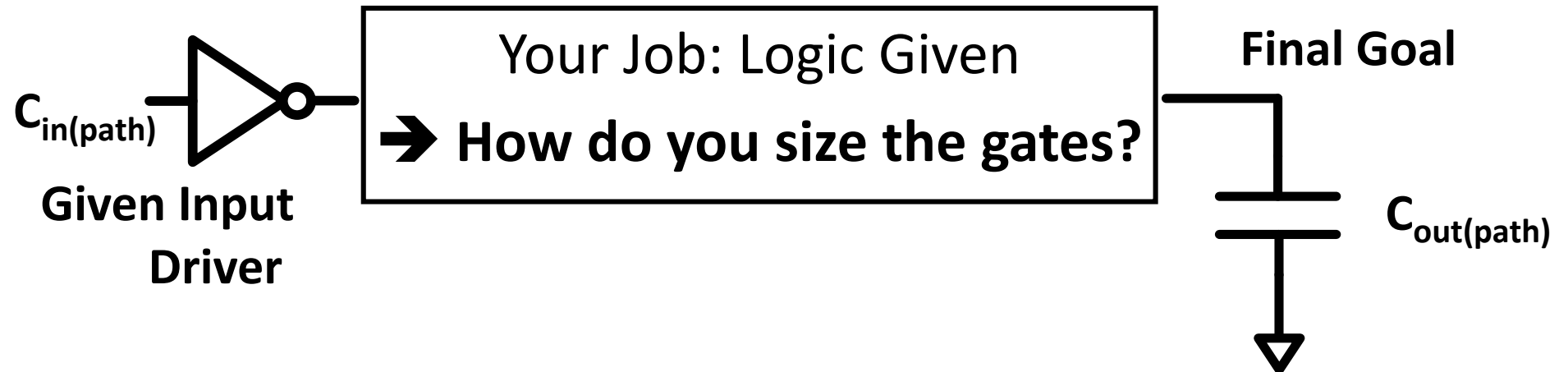- Imagine what situation you possibly be in



Delay in Multistage Logic Networks

 - The number marked in the gates denote C_{in} .



- Then how can you calculate the path delay?

Introducing Path Level Parameters

- There is an incentive to introduce path-level delay parameters that are independent to the each gate size.
- That is, path electrical effort H

$$H = \frac{C_{out(path)}}{C_{in(path)}}$$


- Path logical effort G

$$G = \prod g_i$$

- Path effort

$$F = \prod f_i$$

Need For Branching Effort

 

- Can we say $F = GH$? as in the stage effort case?
- No. What if there are branch paths?
- Thus, to relate F with G and H , we need additional parameter that can characterize branch feature.
- In each stag, branching effort b is defined as

$$b = \frac{C_{onpath} + C_{offpath}}{C_{onpath}}$$

- Path branching effort B is defied as


$$B = \prod b_i$$

- Thus,

$$F = GBH$$

Delay

- You remember

 

$$\text{Path delay } D = \sum d_i = \sum f_i + \sum p_i$$

- If we define *path effort delay* $D_F = \sum f_i$ and *path parasitic delay* $P = \sum p_i$, then

$$D = \sum d_i = D_F + P$$

Minimizing D_F

- Focus on D_F


$$D_F = \sum f_i$$

- We know that $F = \prod f_i$ is constant, no matter how the sizing of each stage is made.
- Let me ask one, when $xy = 2$, what is the minimum of $x + y$?
- When $\prod f_i$ is constant, what is the minimum of $\sum f_i$?
- The sum of numbers whose product is constant is minimized by setting all the numbers equal. Thus, D_F is minimized if all f_i is equal to \hat{f}

$$\hat{f} = g_i h_i = F^{1/N} \quad \rightarrow \text{Gate Sizing Strategy}$$


\rightarrow The minimum delay of the path can be estimated knowing only the N , F , and P without the need to assign transistor sizes.

Minimizing Delay Example

 


The Larger W is, The Faster Circuit is?

 - No. Why?
- Not only current increases, but also its cap increases




Choosing the Best Number of Stages

 - Is smaller N always results in smaller delay?



N	1	2	3	4
f	64	8	4	2.8
D	$64+1$	$16+2$	$12+3$	$2.8*4+4$

Generally, We Can Change N Easily

 

- After N is determined, you can choose $f = F^{1/N}$ to minimize the delay. Question is how to determine N . Strategy?
- Express D in terms of N then differentiate it with respect to N .


$$D = NF^{1/N} + P = NF^{1/N} + \sum_{i=1}^{n_1} p_i + (N - n_1)p_{\text{inv}}$$

- Differentiating with respect to N , and defining $\rho = F^{1/\hat{N}}$

$$\begin{aligned} \frac{\partial D}{\partial N} &= -F^{1/N} \ln F^{1/N} + F^{1/N} + p_{\text{inv}} = 0 \\ \Rightarrow p_{\text{inv}} + \rho(1 - \ln \rho) &= 0 \end{aligned}$$


Solving Numerically,

 - D becomes minimized when $\rho = F^{1/N} \doteq 3.6$




- Using a stage effort of 4 is a convenient choice and simplifies mentally choosing the best number of stages.
- This effort gives delays within 2% of minimum for p_{inv} in the range of 0.7 to 2.5. \rightarrow FO4 is representative sizing strategy.

Implementing 4 to 16 Decoder

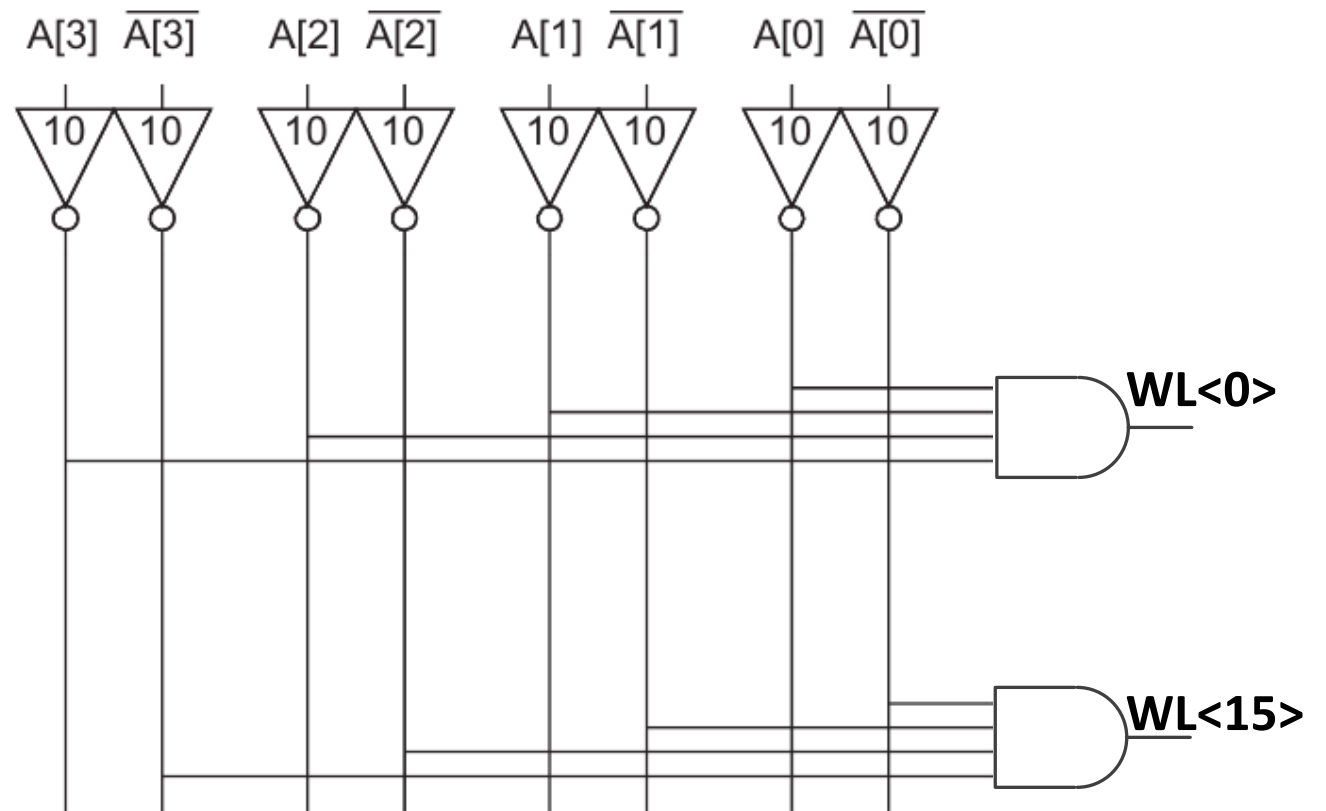

Implementing Decoder

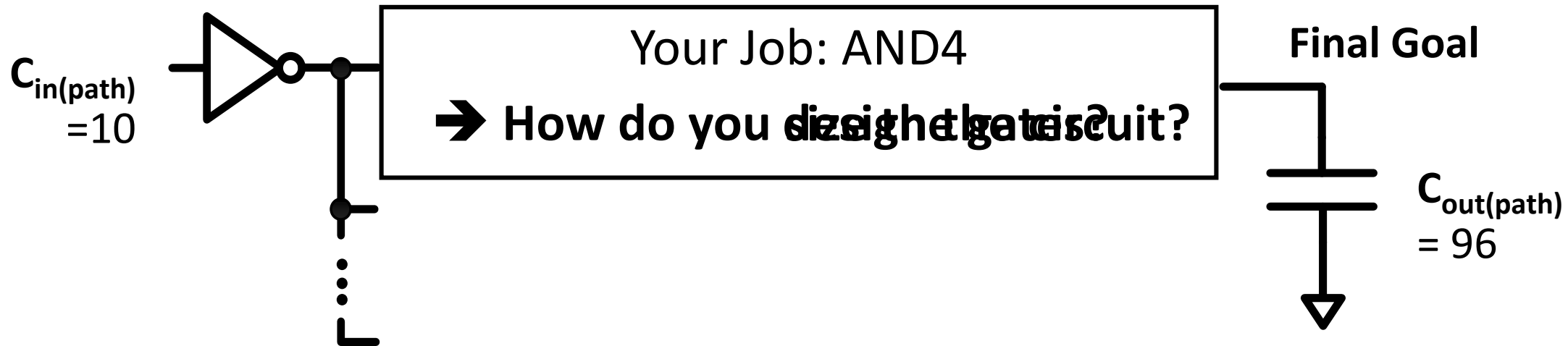

Comparing Designs

Design	Stages N	G	P	D
NAND4-INV	2	2	5	29.8
NAND2-NOR2	2	20/9	4	30.1
INV-NAND4-INV	3	2	6	22.1
NAND4-INV-INV-INV	4	2	7	21.1
NAND2-NOR2-INV-INV	4	20/9	6	20.5
NAND2-INV-NAND2-INV	4	16/9	6	19.7
INV-NAND2-INV-NAND2-INV	5	16/9	7	20.4
NAND2-INV-NAND2-INV-INV-INV	6	16/9	8	21.6

Summary

Term	Stage Expression	Path Expression
number of stages	1	N
logical effort	g (see Table 4.2)	$G = \prod g_i$
electrical effort	$h = \frac{C_{\text{out}}}{C_{\text{in}}}$	$H = \frac{C_{\text{out(path)}}}{C_{\text{in(path)}}}$
branching effort	$b = \frac{C_{\text{onpath}} + C_{\text{offpath}}}{C_{\text{onpath}}}$	$B = \prod b_i$
effort	$f = gh$	$F = GBH$
effort delay	f	$D_F = \sum f_i$
parasitic delay	p (see Table 4.3)	$P = \sum p_i$
delay	$d = f + p$	$D = \sum d_i = D_F + P$

Another Thing, Critical Path

- Almost paths are already fast enough for the timing goals of the system.
- However, there are critical paths that limit the speed of the system

