

Power (1)

Hanwool Jeong

hwjeong@kw.ac.kr

Contents

- Introduction
- Dynamic Power
- Static Power

Same Battery Capacity



Talk Time : 22.9 Hours




Talk Time : 24.5 Hours

Introduction


- ✓ What is power? Why is it important? How is it determined?

Work & Energy in Physics

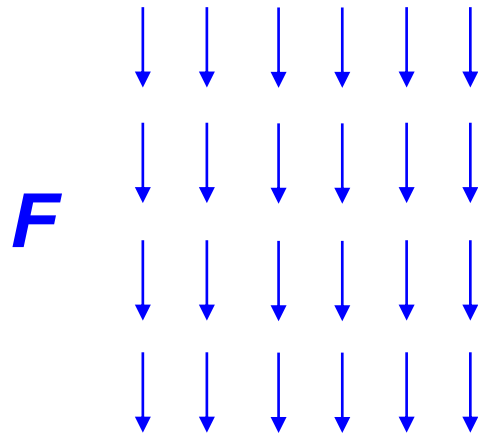
- **Work?** → $W = \int F ds$ or $W = Fs$ (when F is fixed over s)
- **Energy** is the capacity for doing **work**.
- We can say “**energy**” is **dissipated or consumed** to do something we can call “work”



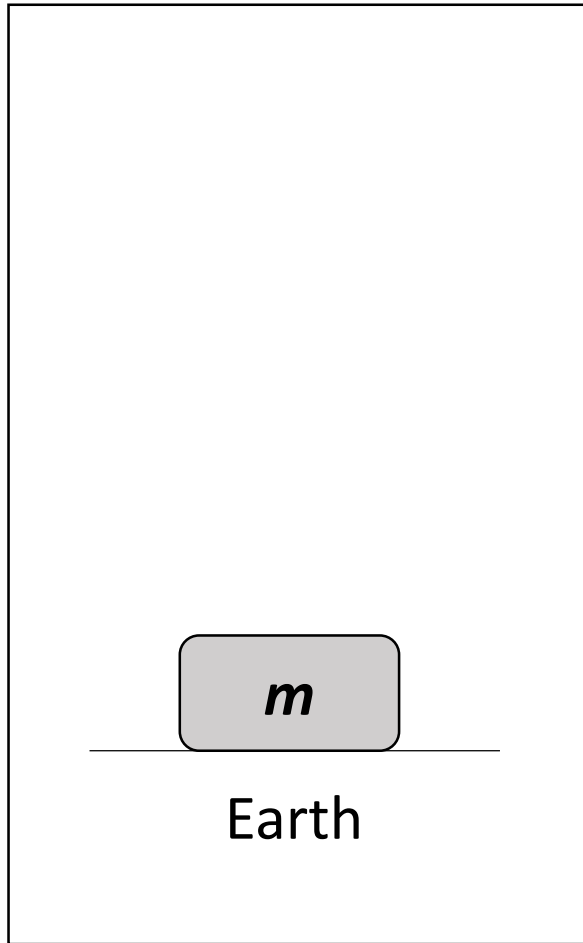
Which is More Natural? Or Which Does Have More Energy?




vs.

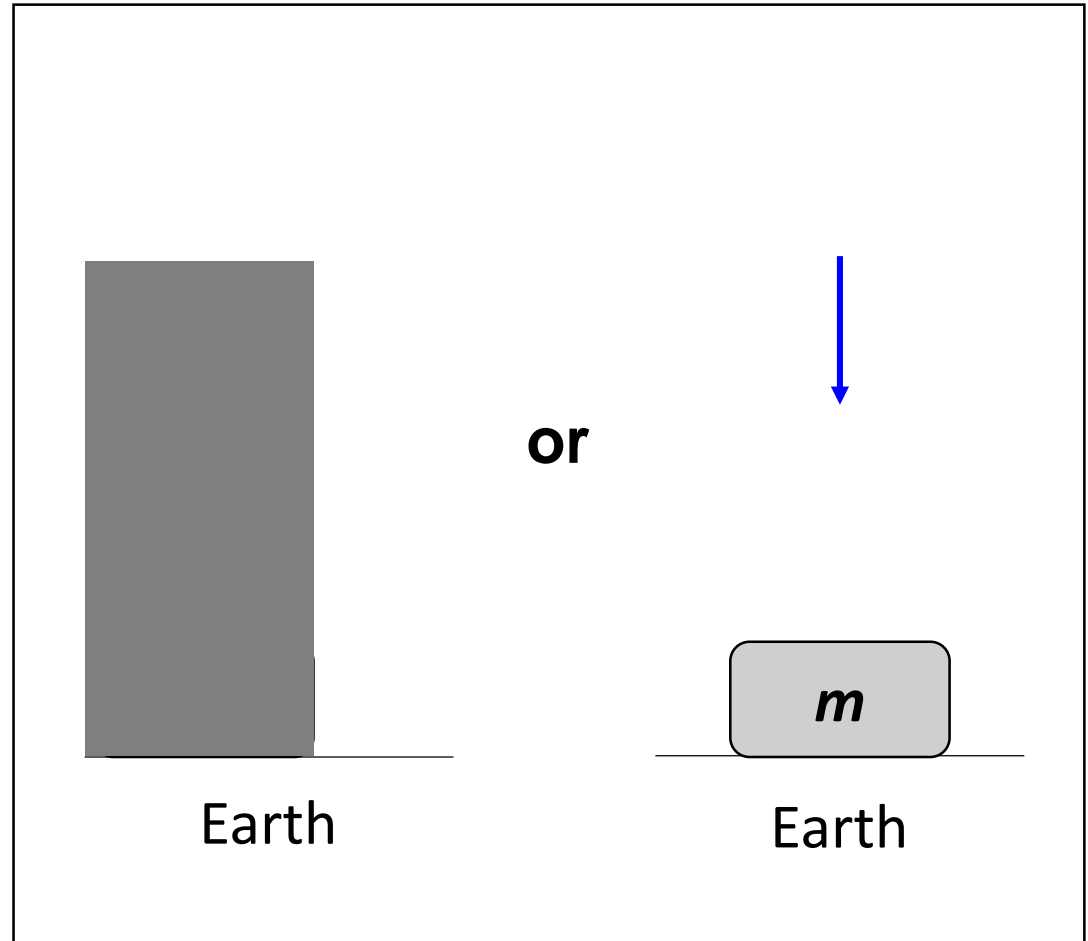

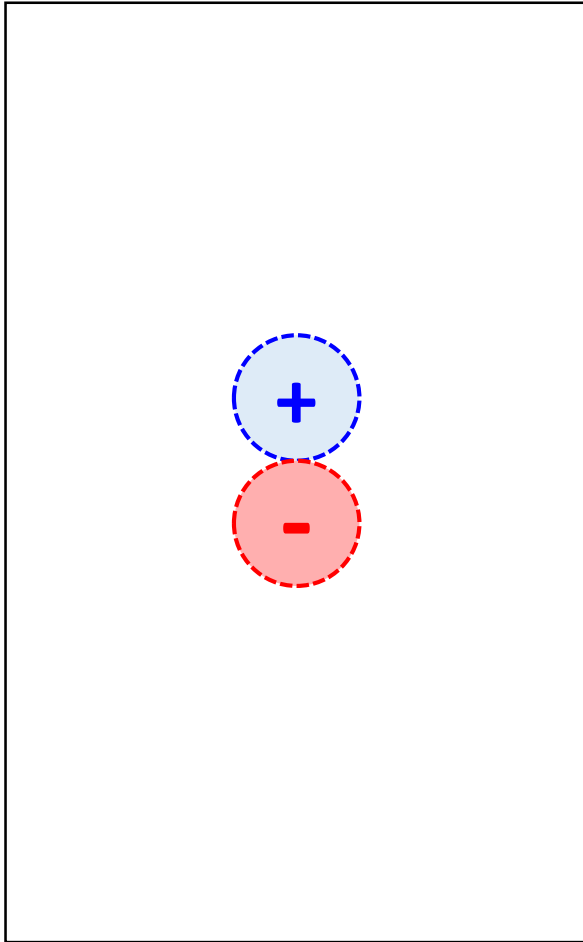Again, Which is More Natural? or Which Does Have More Energy?




VS.

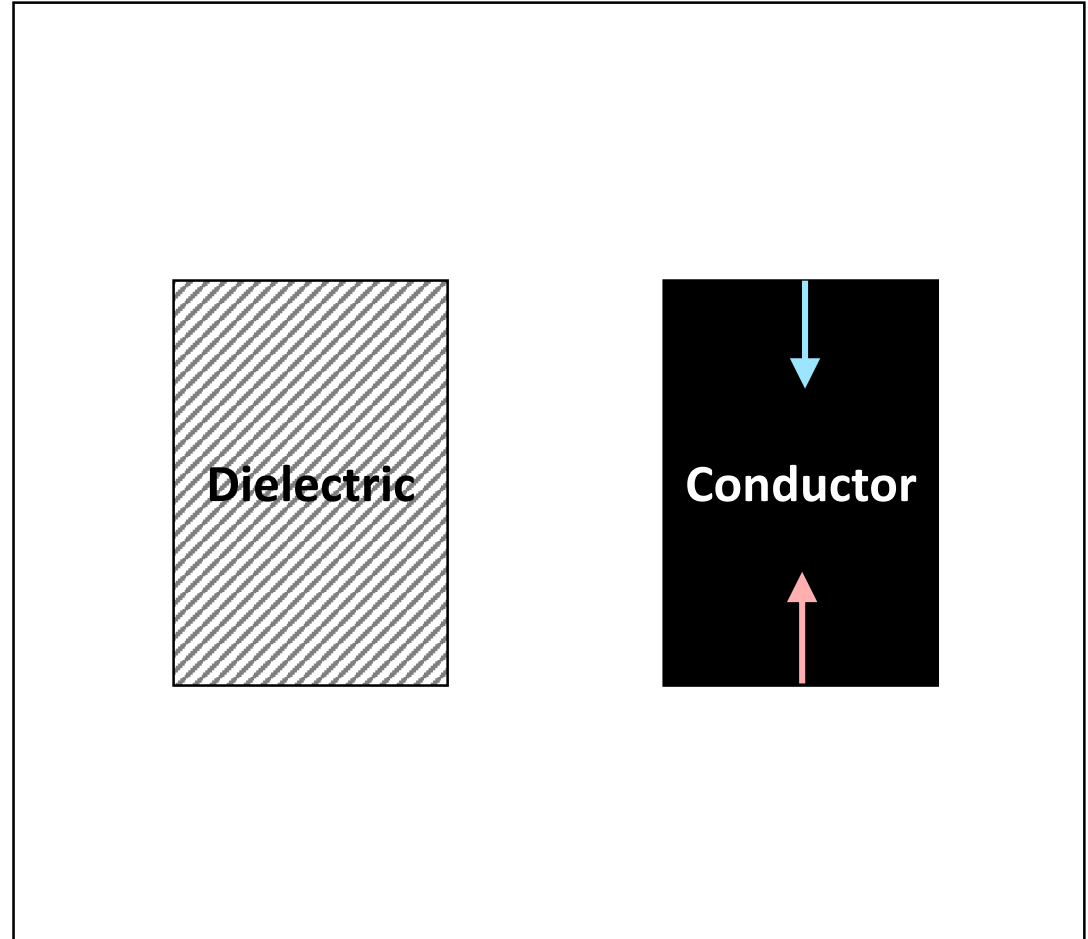


More Familiar/Simple Situation; Applying “Field” → Charge Moves

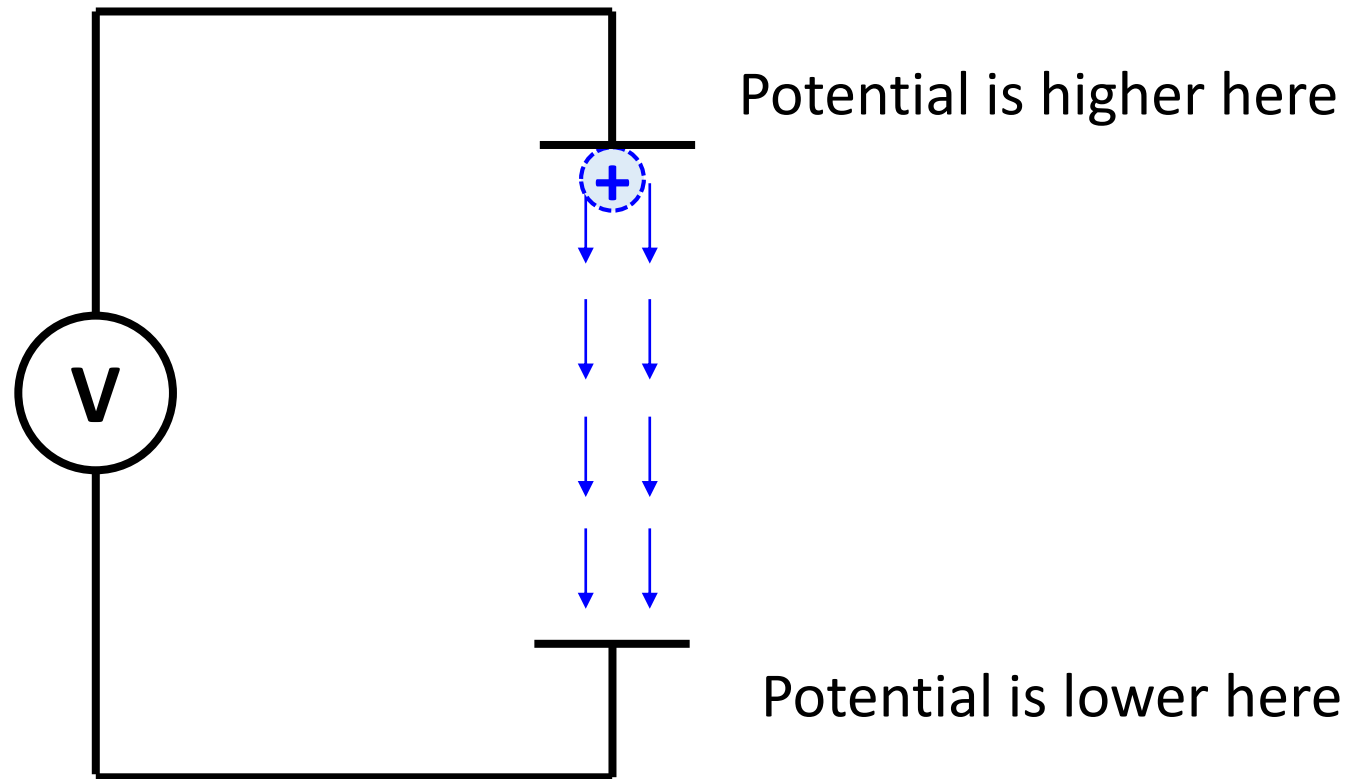- Voltage is given → Electric field is applied
- Then, charge becomes capable of moving, responding to the field



Meaning of Charge Movement for Voltage

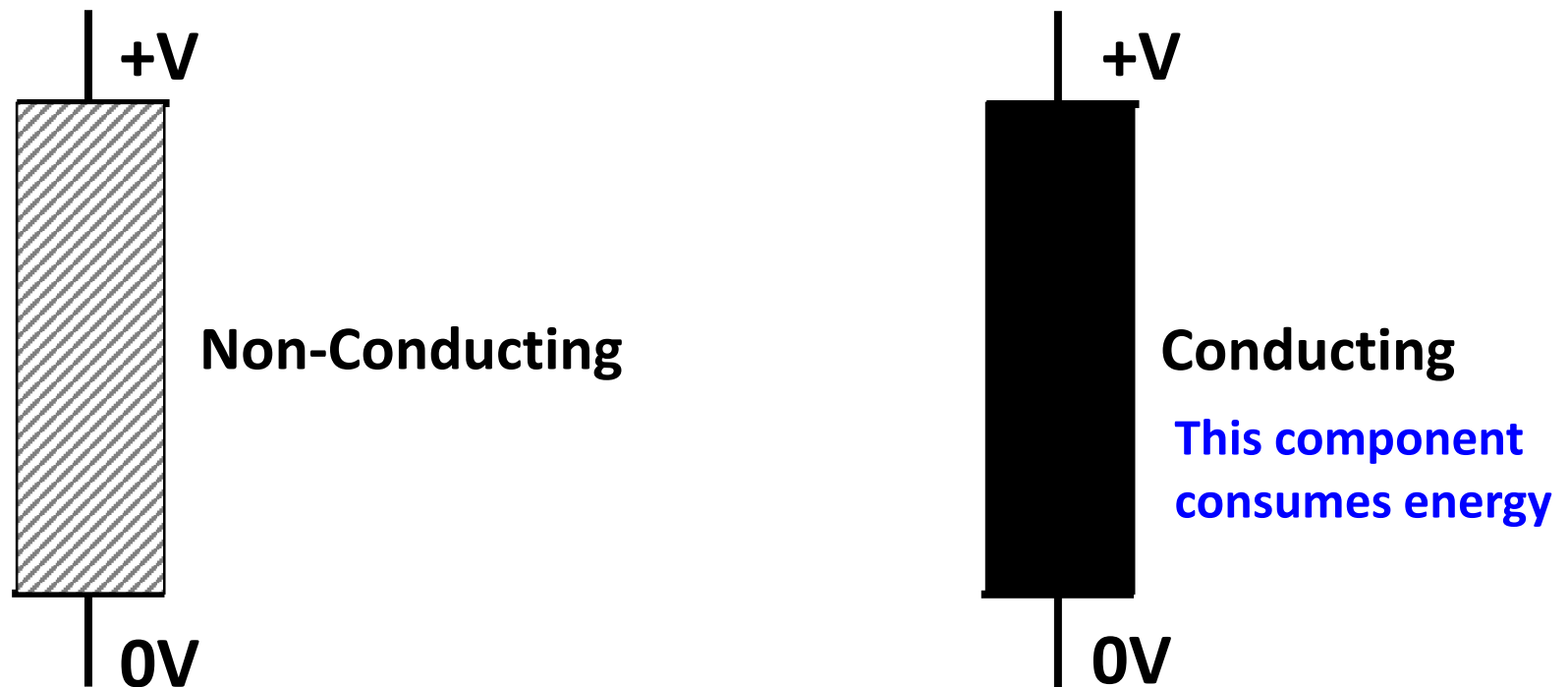
- Potential of charge is decreased
 - Corresponding amount of the energy is converted to something else
- ➔ We can say the energy is consumed by the component.



Dominant Energy Consumption Source in Conduction; Drift

- You remember drift current?

$$v = \mu E$$

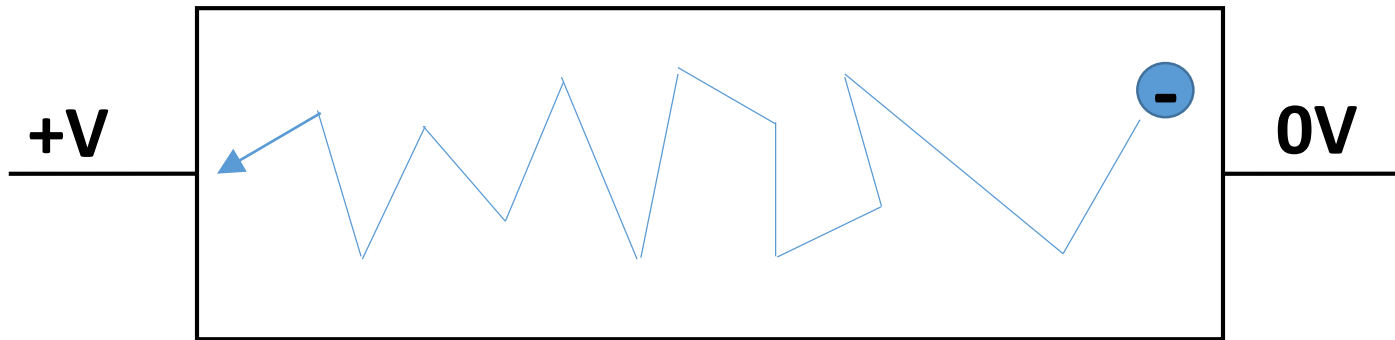

Conducting Drift Current Means Energy Dissipation

- By how much? Consider the definition of voltage
- Then how can you relate it with **current**?

$$E_{\text{consumed}} = \Delta W = QV = IVt$$

Power
= Energy per time
= $I \times V$





Conducting

**This component
consumes energy**

Electrical Energy in Digital Circuit

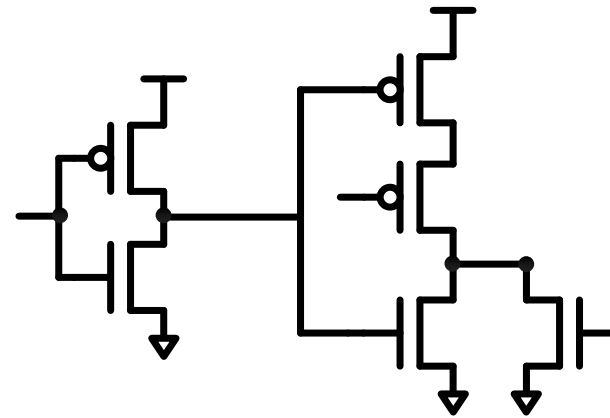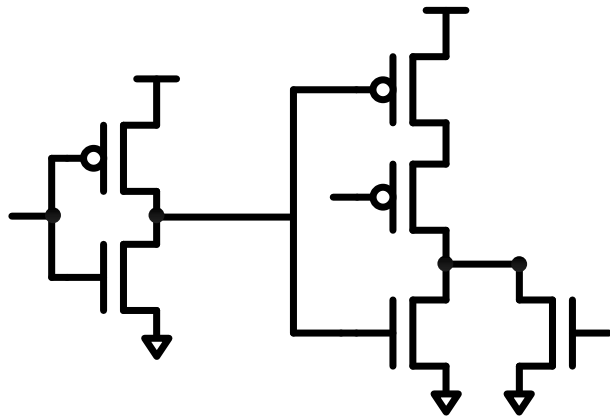- Charging & discharging nodes to VDD and GND, respectively.
➔ Key operation of digital circuits



Formal Definitions

- Instantaneous power consumed or supplied at time t

$$P(t) = I(t)V(t)$$

- Energy consumed or supplied over some time interval T ,

$$E = \int_0^T P(t) dt$$

- Average power over the interval

$$P_{\text{avg}} = \frac{E}{T} = \frac{1}{T} \int_0^T P(t) dt$$

Examples


- The power dissipated in the resistor is

$$P_R(t) = \frac{V_R^2(t)}{R} = I_R^2(t)R$$



- The power supplied by the voltage source is


$$P_{VDD}(t) = I_{DD}(t)V_{DD}$$

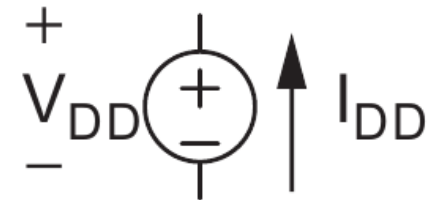

- When the capacitor is charged from 0 to V_C , how much energy stored?

CMOS Inverter

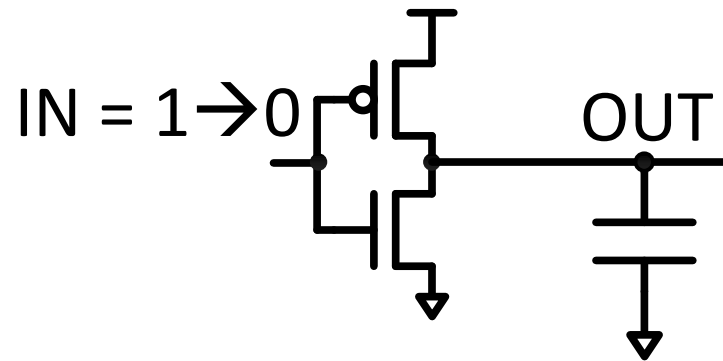
- Suppose that the output capacitance is C_{out} .
- What if IN falls? How about IN rises?



$C_{out} : 0 \rightarrow V_{DD} \rightarrow E_C?$

Power Supplied from V_{DD} ?

pMOS dissipates :

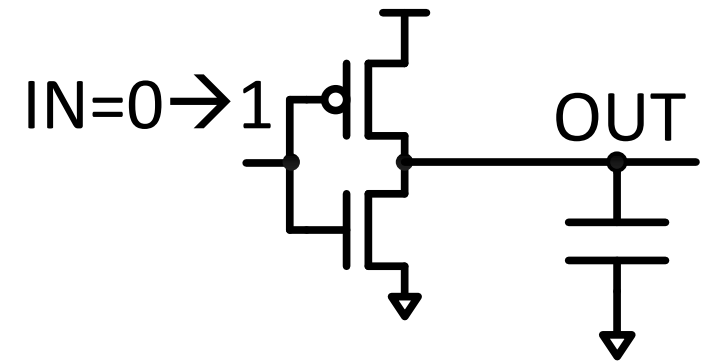

$C_{out} : V_{DD} \rightarrow 0 \rightarrow E_C?$

nMOS dissipates :

\rightarrow Short-circuit current path exist. Why?

Dynamic Power & Static Power

- Dynamic power is power required for switching the load capacitors.
- Even when the gate is not switching, it draws some static power.
 - ➔ Because an OFF transistor is leaky, a small amount of current I_{static} flows between power and ground, resulting in a static power dissipation

Sources of Power Dissipation

- Dynamic power dissipation come from:
 - 1) Charging and discharging load capacitances as gates switch
 - 2) “short-circuit” current while both pMOS and nMOS stacks are partially ON

$$P_{\text{dynamic}} = P_{\text{switching}} + P_{\text{short circuit}}$$

- Static power dissipation come from:
 - 1) Subthreshold leakage through OFF transistors
 - 2) Gate leakage through gate dielectric
 - 3) Junction leakage from source/drain diffusions
 - 4) Contention current in ratioed circuits

$$P_{\text{static}} = (I_{\text{sub}} + I_{\text{gate}} + I_{\text{junct}} + I_{\text{contention}})V_{DD}$$

$$P_{\text{total}} = P_{\text{dynamic}} + P_{\text{static}}$$