

# Logic Circuit Families (2)

Hanwool Jeong

[hwjeong@kw.ac.kr](mailto:hwjeong@kw.ac.kr)

# Contents


- Pseudo nMOS
- Cascode Voltage Switch Logic
- **Dynamic Circuit and Domino Logic**
- Pass-Transistor Circuits

# Dynamic Circuit and Domino Logic

- ✓ Replacing always-pull-up of pseudo nMOS with “clocked” pull-up

 
# Combinational Circuits vs. Sequential Circuits

- Combinational circuit: output is a function of the current inputs.
- Sequential circuit: output depends on **previous** as well as **current** inputs; such circuits are said to have state.
- Sequential logic is essential for today electronic system  
(Have you heard of pipeline or finite state machine?)





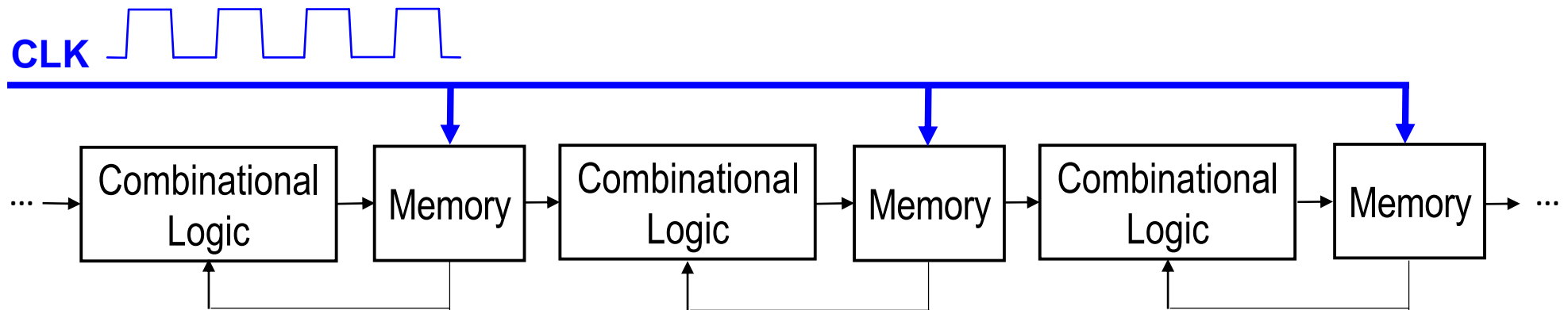
# “Synchronous” Sequential Circuit

- The state of device changes only at discrete times dominated by a “clock” signal.




➔ Besides the main CLK signal, many other dynamically changing “control” signals can be generated

# Dynamic Inverter Utilizing Clocked Pull-up

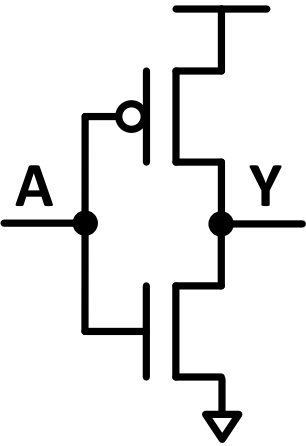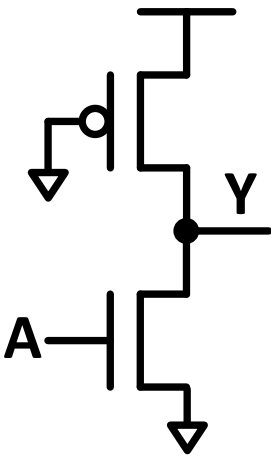
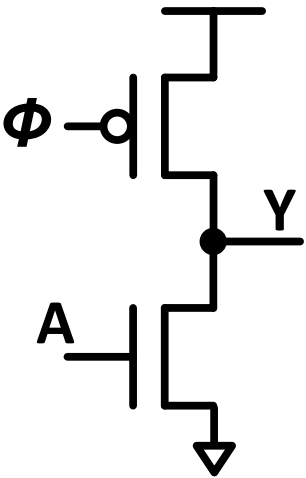
Static CMOS	Pseudo NMOS	Dynamic
		

 Operated in two phases:  
1) Precharge and 2) Evaluation





  
# Dynamic Logic Gate

- Precharge ( $\phi=0$ )
  - Clocked pMOS is ON, initializing Y high.
- Evaluation ( $\phi=1$ )
  - Clocked pMOS is turned off
  - Y may remain high or be discharged low according to pulldown network controlled by inputs.
- Why is it faster than CMOS gate? Area?
- No static power as pseudo-nMOS.





# Various Dynamic Logic Gates

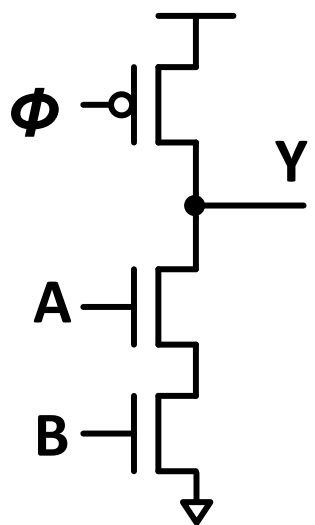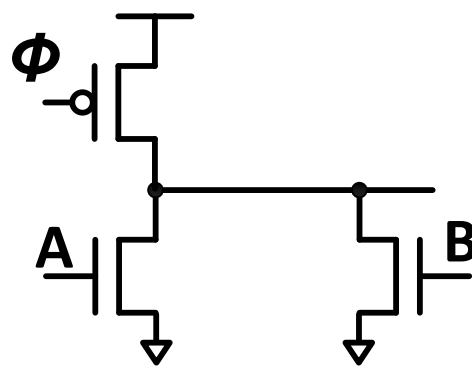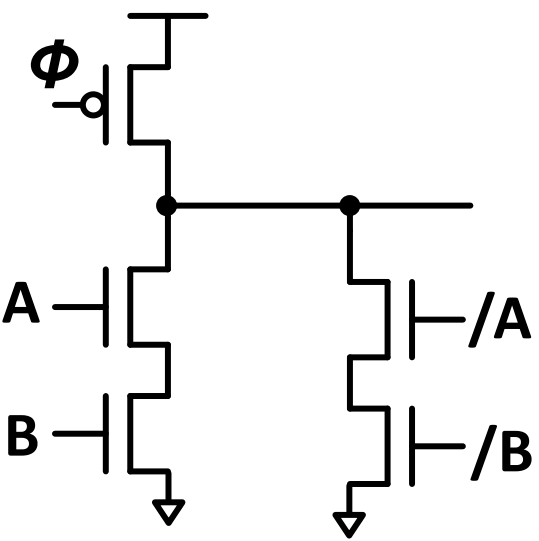NAND2	NOR2	XOR2
		



# Can You Find Potential Problems?

  - 1) During precharge, there might be contention.
- 2) If A falls during evaluation, Y cannot be raised.  
(Monotonically falling output, monotonicity problem)



What would Y be like?




# How Can You Resolve Contention Problem?

- State your goal verbally and specifically.

**“When  $\Phi = 0$ , the pull-down network should be disabled.”**

Condition : MOSFET gate node

Operation : MOSFET drain current

   

**Footed Dynamic Inverter**



# Footed Dynamic Gates

- Width needs to be increased to achieve equal speed

	NAND2	NOR2	General logic
Unfooted			
Footed			

  
# How Can You Handle Monotonicity Problem?

- What is the cause of the problem?
  - ➔ **A** falls during the evaluation.
  - ➔ Can't we force **A** only to **rise** or **kept low** during evaluation?
  - ➔ Can't we make **A** **monotonically rising** during evaluation?


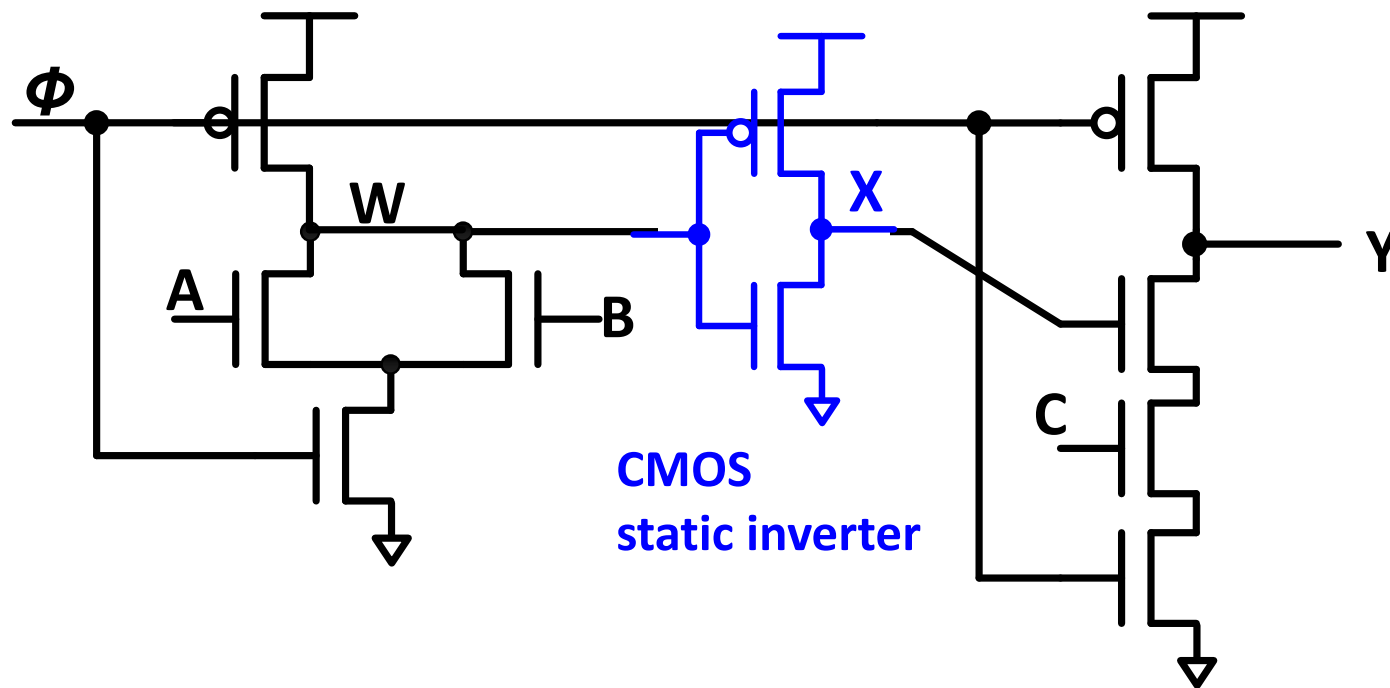
# How Can We Achieve an Input “Monotonically Rising” During Evaluation


- Dynamic gate output is **monotonically falling** during evaluation
- ➔ Then, we can easily achieve a signal monotonically rising during evaluation by



# Domino Logic Gate

- Domino logic = Dynamic gate + static inverter



Domino OR

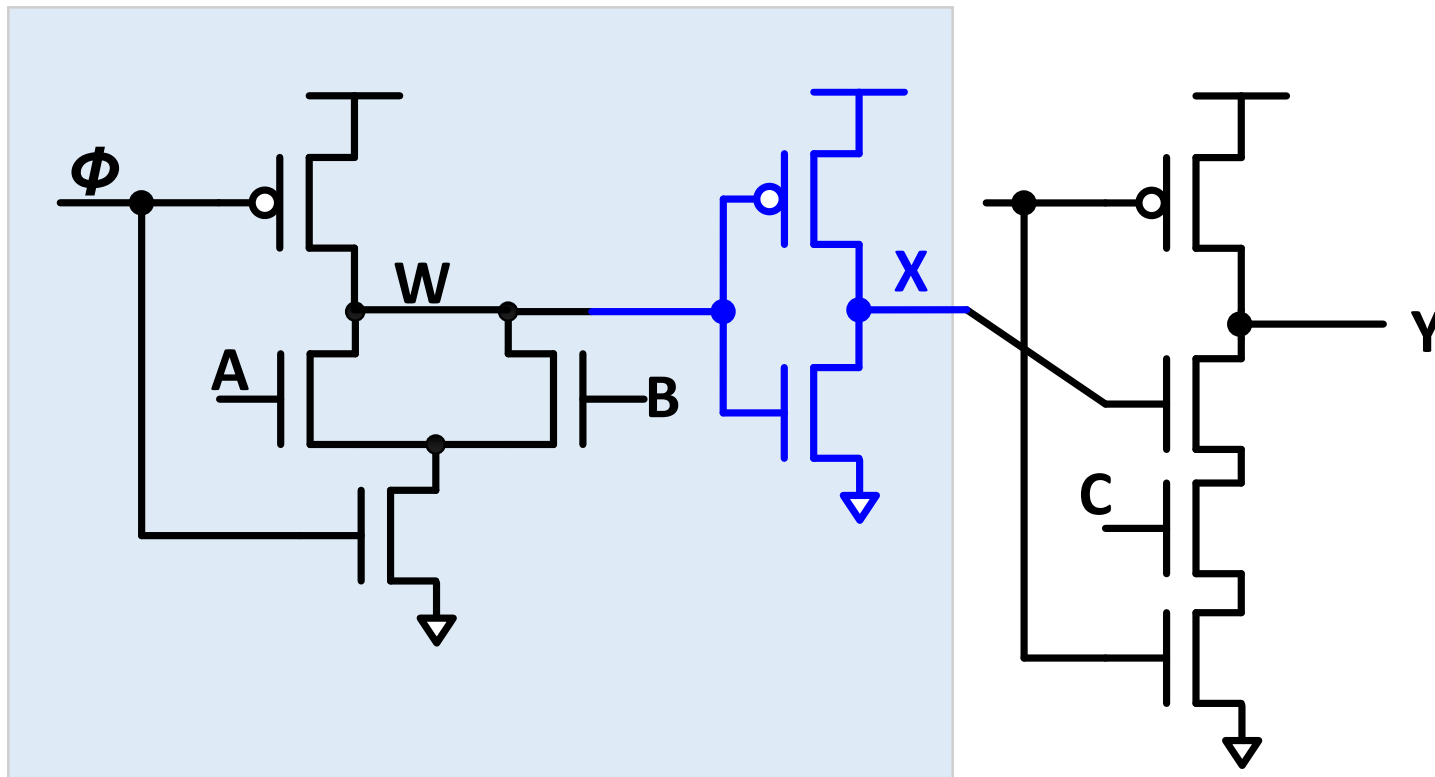


# Operational Waveform

- Monotonicity problem is solved

Domino OR

 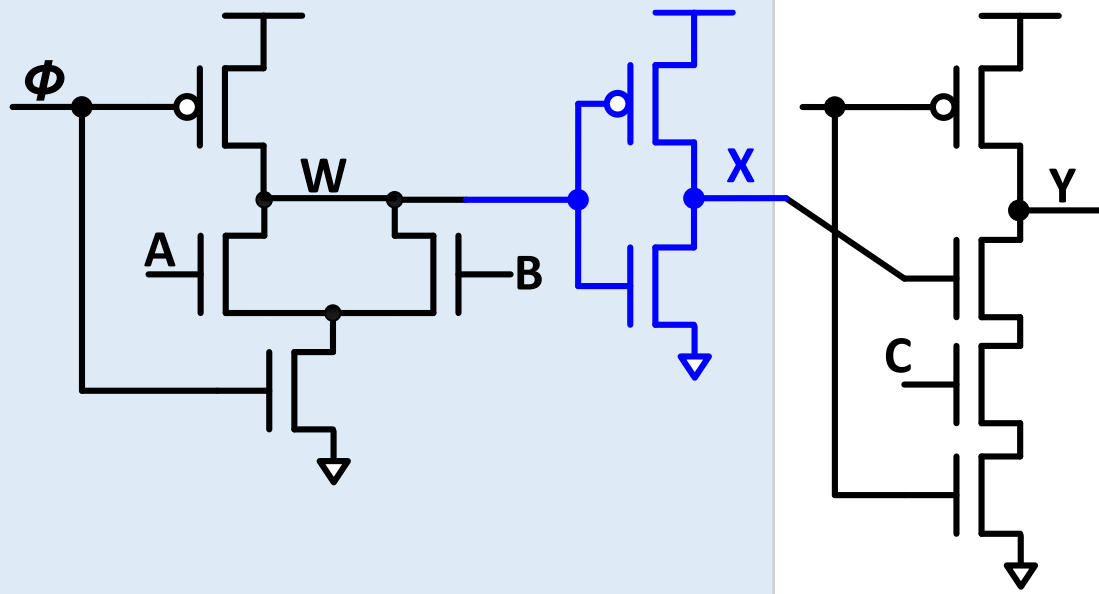

# 8:1 MUX Using Domino Logic

 





# Potential Problem for $A = 0$

3) When  $A = 0$ ,  $Y$  is floating high.


➔ “When Y is high, Y should be driven to  $V_{DD}$ .”

➔ Who can drive Y to  $V_{DD}$ ?

  
 
# Keeper Implementation for Noise Robustness

- Note that keeper pMOS should be sufficiently weak.



# Summary

- Clocked pull-up + pull-down network for logic implementation
- Contention during precharge can be solved through footed circuit
- Monotonicity problem is resolved by domino logic
- Keeper can be utilized to prevent output floating of the dynamic gate, but the strength should be carefully determined.