

Logic Circuit Families (3)

Hanwool Jeong

hwjeong@kw.ac.kr



Contents

- Pseudo nMOS
- Cascode Voltage Switch Logic
- Dynamic Circuit and Domino Logic
- **Pass-Transistor Circuits**


Pass TR Logic Basic

- ✓ Motivation for using pass TR circuits
- ✓ Applying to MUX design

Pass TR vs. Transmission Gate

  



Pass
Transistor

 

Transmission
Gate

  
2:1 MUX Implementation

- Pass TR or TG can play a good role for achieving tri-state.




Key Difference of Pass TR from Other Logic Families

 - A single TR accepts 2 inputs to determine 1 output.
- **Chance** to reduce the number of TRs for **MUX** implementation.




A	B	Y
0	0	Z
0	1	0
1	0	Z
1	1	1

 

A	B	Y
0	0	Z
0	1	0
1	0	Z
1	1	1-

Is there any way to restore $1-(V_{DD}-V_{th})$ into full V_{DD} ?

4:1 MUX Example

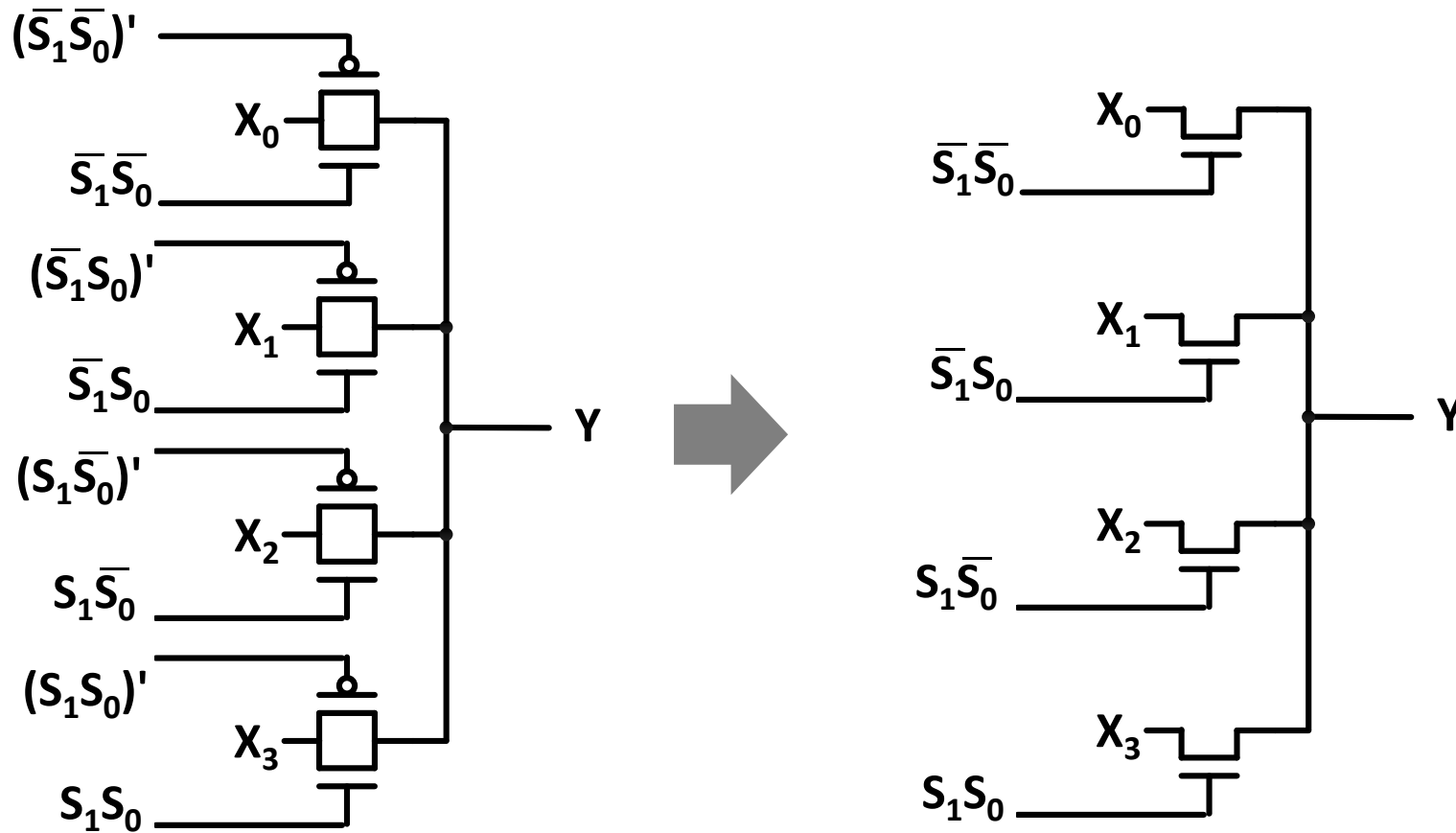


Revisit the Role of Cross-Coupled PFET


- You also saw this structure in the level shifter
- It operates in the positive feedback manner.

➔ We can use cross-coupled pFETs for amplification/restoring

 ➔ This generalization thinking is so important!




Level Shifter

 


CVSL

Ideation Procedure

 - 1) Replacing TG/tri-state inverter with pass TR in MUX **to reduce the number of transistors**
- 2) Employing the cross-coupled pFET **to restore weak “1” to strong “1”**





Design Procedure

 

Complementary Pass Transistor Logic (CPL)


K. Yano, et al, "A 3.8-ns 16×16 -b multiplier using complementary pass-transistor logic," JSSC, vol. 25, no. 2, Apr. 1990, pp. 388–395

  Mitigating Drivability Problem in CPL MUX



Can't We Use PMOS Pass TR?

- Sure! Why not?

 



XOR-XNOR Design

- ✓ Reducing the TR number thru Pass TR Logic
- ✓ Potentially decreases area, energy, and delay

Previous XOR2 Designs


A	B	Y
0	0	0
0	1	1
1	0	1
1	1	0

- $Y = \bar{A}B + A\bar{B}$

  


Key Difference of Pass TR from Other Logic Families

 - A single TR accepts 2 inputs to determine 1 output.
- **Chance** to reduce the number of TRs for **logic** implementation.



A	B	Y
0	0	Z
0	1	0
1	0	Z
1	1	1-

$$Y = AB \text{ (when } B=1\text{)}$$

 


$$Y = A_0 \bar{B} + A_1 B$$

We can achieve XOR2!



$$Y = A\bar{B} + \bar{A}B$$

CPL based XOR Design

 

Comparing it With CVSL

- Could be faster in CPL (Why?)

 
 


How About This?

- With the output driver (inverter), full VDD output can be achieved (Think of the restoring feature of the inverter!)



→ Yes.. but It incurs the short-circuit current at the output inverter.

→ Can you improve it?

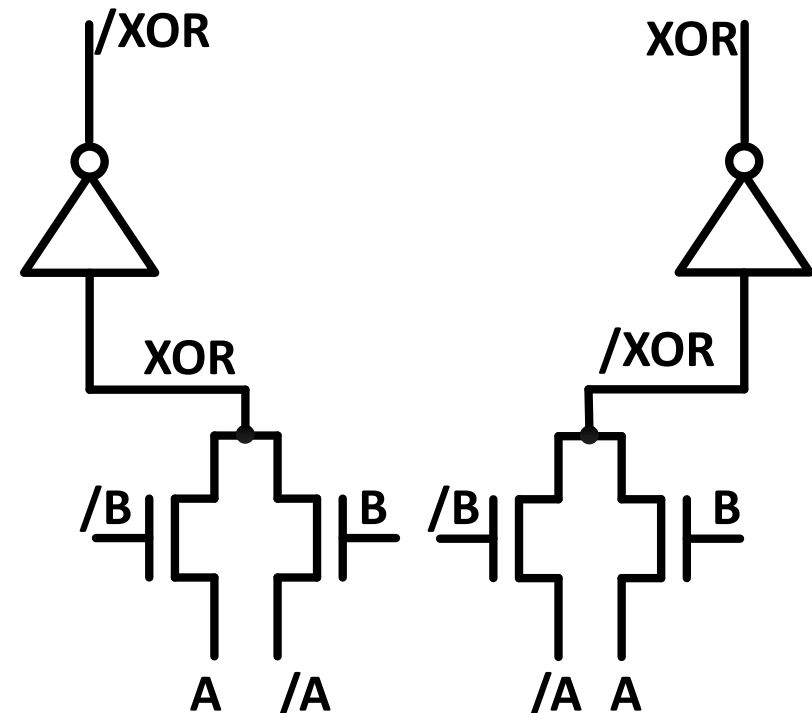 



CMOSTG Design

  - We can use TG instead of pass TR \rightarrow CMOSTG
- Is there any other way to make it full V_{DD} ?



Ideation

  - 1) \neg XOR node should be pulled up → We should utilize PMOS
- 2) When? Condition formed by A and B is meaningless → Equivalent to CMOSTG
- 3) Again, when? utilizing XOR! When XOR = 0
- 4) Thus, we can add pull-up pMOS to \neg XOR that is controlled by XOR.





**Lean Integration
with Pass Transistors
(LEAP)**

K. Yano, Y. Sasaki, K. Rikino, and K. Seki, "Top-down pass-transistor logic design," JSSC, vol. 31, no. 6, Jun. 1996, pp. 792–803.

LEAP is Slow

  
- 1) Why? \neg XOR is pulled up solely by A or \neg A while, in the CPL, the opposite path aids to charge up \neg XOR.
- 2) In addition, complementary output is often useful.

➔ Is there any way to reduce TR number of CPL without removing the operation complementary output?



Ideation

 - 1) Cross-coupled pFET is removed.
- 2) Try to find which part can be utilized to replace the cross-coupled pFET
- 3) What is the role of the cross-coupled pFET?
→ It is to charge up Y and /Y when required.
- 4) When? Y should be charged up when XOR is raised.





Swing-Restored Pass Transistor Logic (SRPL)

  A. Parameswar, H. Hara, and T. Sakurai, "A swing restored pass-transistor logic-based multiply and accumulate circuit for multimedia applications," JSSC, vol. 31, no. 6, Jun. 1996, pp. 804–809.


Limitation of SRPL

- Suppose that Y is supposed to be pulled down as $A=0$ and $B=0$, while $(Y, /Y)$ initially is $(1, 0)$
- Contention occurs at the both sides, increasing the power and delay.



Ideation; Contention Mitigation

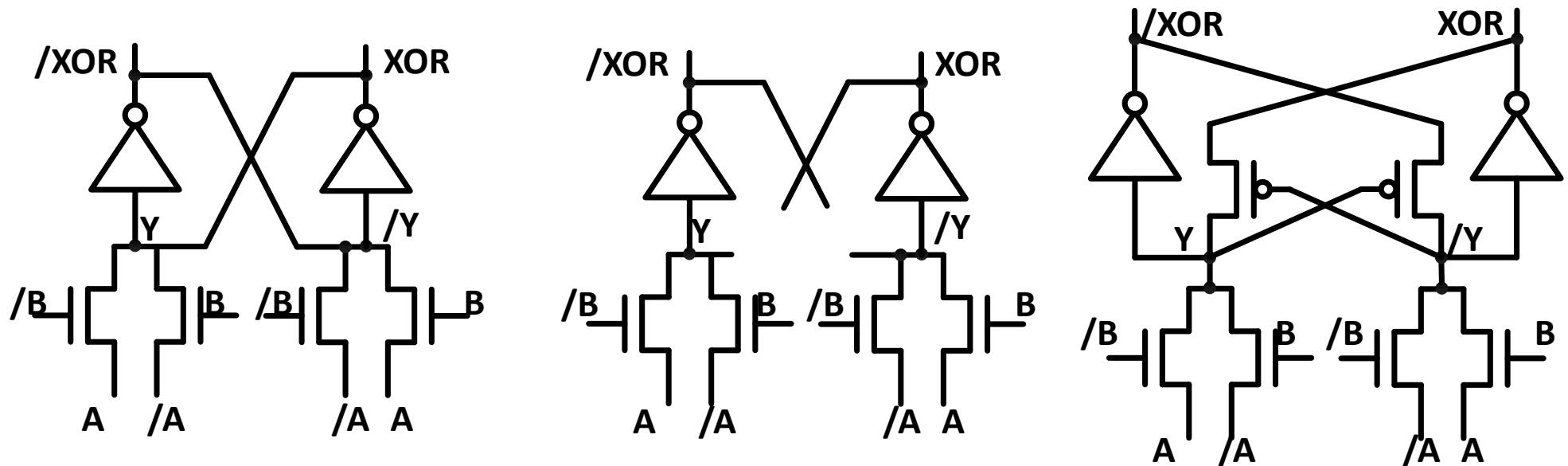- 1) How can we make A or /A can easily pull down Y or /Y?
- 2) Not directly connect output of inverter to Y.
- 3) But we should keep the original goal being achieved, that is, pulling up Y to full VDD.
- 4) Is there any way pull-up VDD to full, while not disturbing Y pull-down?





M. Song, G. Kang, S. Kim, and B. Kang, "Design methodology for high speed and low power digital circuits with energy economized pass-transistor logic (EEPL)," Proc. 22nd European SolidState Circuits Conf., 1996, pp. 120–123.

Energy Economized Pass Transistor Logic (EEPL)

PMOS Pass TR + Cross-Coupled NMOS

  
- Can't we make XOR/XNOR only with A and B? (i.e., without /A and /B)?
- We can go on by relying on the facts that
 - 1) NMOS with A-B can generate XNOR and pMOS with A-B can generate XOR (highlighted below) → but output can be imperfect for some cases.
 - 2) XOR can be used to restore XNOR and vice versa.



Ideation

- Constraint: Don't use $\neg A$ and $\neg B$

A	B	XOR	XNOR
0	0	0	1
0	1	1	0
1	0	1	0
1	1	0	1

 


How about when $B = 1$?


- 1) $A=0$: XOR=1
- 2) $A=1$: XOR=0

$B=0$ is problematic here

 - 1) $A=1$: XNOR = 0
- 2) $A=0$: XNOR = 1




Resultant 8T XOR-XNOR

 

Jinaping Hu, International Journal of Advancements in Computing Technology, 2012

Ideation Again

 

A	B	XOR	XNOR
0	0	0	1
0	1	1	0
1	0	1	0
1	1	0	1

B = 1 : problem

1) A=0 : XOR=1

2) A=1 : XOR=0

→ XNOR can restore this

B = 0 : problem


1) A=1 : XNOR=0

2) A=0 : XNOR=1

→ XOR can restore this

Resultant 6T XOR-XNOR

 - Can you find the limitation?
- ➔ Due to V_{th} drop of gate level of P3 and N3, restoring is very slow




D.Radhakrishnan, IEEE Proc.-Circuits Devices Syst., 2001

Accelerating Restoring


- Let's focus on XOR.

A	B	XOR	XNOR
0	0	0	1
0	1	1	0
1	0	1	0
1	1	0	1

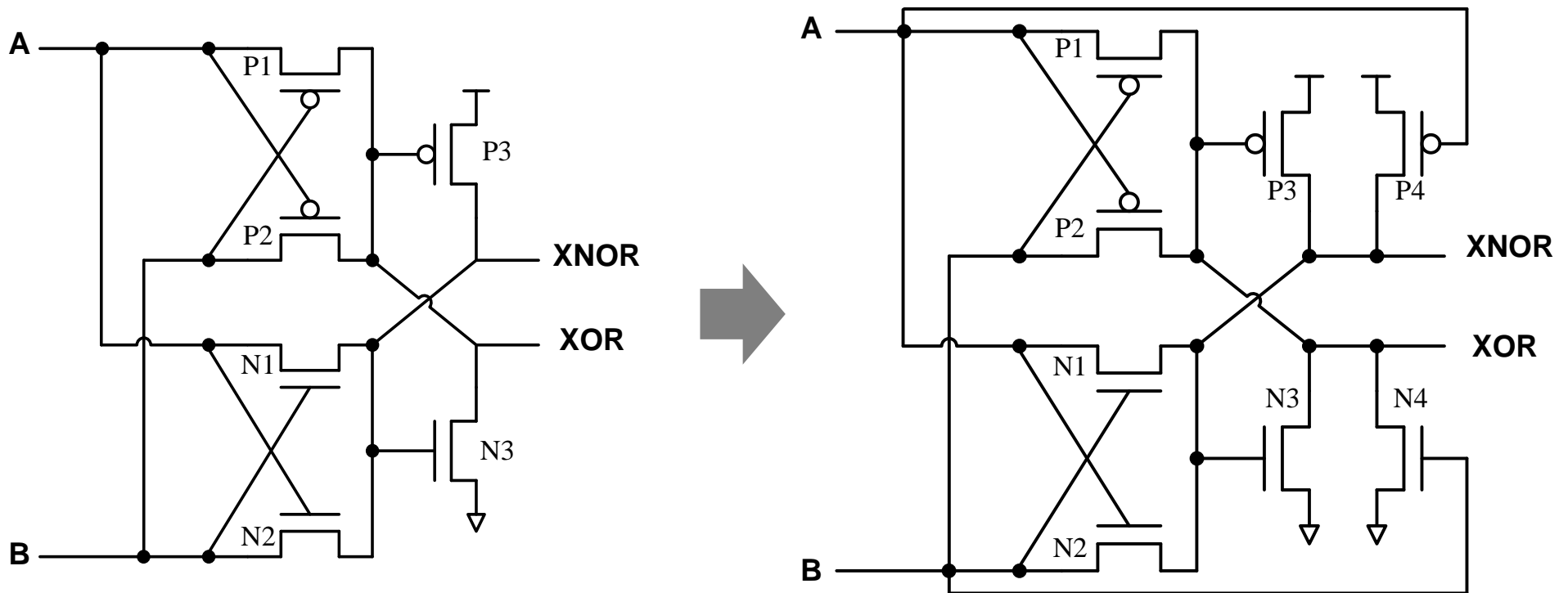


Resultant 8T XOR-XNOR

 - Can you find the limitation?
- ➔ How can you solve the contention issue?



M. Elgamel, Great Lakes symposium on VLSI, 2003

Resultant 10T XOR-XNOR

 

M. Zhang, ISCAS2003

Summary

- Pass TR can be used to implement logic to reduce the number of transistor, leading to reduction in area/energy/delay.
- Various methods for designing XOR2 and XNOR2 are described to resolve the limitation of the previous structure in terms of area/energy/delay.
- Step by step ideation procedure is highly important.